

# Linear Variable Differential Transformers—Lab 14

M.V. Iordache, *EEGR2051 Circuits and Measurements Lab*, Fall 2019, LeTourneau University

See <https://mviordache.name/EEGR2051> for more information.

## LINEAR VARIABLE DIFFERENTIAL TRANSFORMERS

### OBJECTIVES:

- Demonstrate the operation of an LVDT and obtain its operation curve.
- Obtain graphs showing the dependence of the mutual inductance on the displacement of the core.
- Continued familiarization with the oscilloscope and correct grounding techniques.

REFERENCE: Student Reference Manual for Electronic Instrumentation Laboratories, Chapter 14.


### EQUIPMENT:

- One LVDT.
- One  $47\Omega$  resistor with binding posts (from the cabinet).
- One waveform generator.
- One oscilloscope.
- One digital multimeter (DMM)


### PROCEDURE:

1. Set the waveform generator for a high impedance output load (HiZ), and a 100 kHz sine waveform of 63 mV peak-to-peak.
  2. Press *Default Setup* on the front panel of the oscilloscope.
  3. Visualize the sinewave on the oscilloscope. Adjust vertical sensitivity so that the waveform has at least 4 divisions on the vertical.
  4. Press *Cursors* to activate the cursor functions of the oscilloscope.
  5. The cursor functions are useful for **precise** measurements. Measure the peak-to-peak value of the signal using cursors. Be precise.  $V_{pp} = \underline{\hspace{2cm}}$
  6. The oscilloscope also provides automatic measurement functions that are useful for performing **quick** measurements. Such measurements are typically not as precise as the manual measurements performed with cursors. For best results:
    - a. Ensure that the signal fits on the screen and covers at least a few vertical divisions.
    - b. Ensure that at least one or two periods of the signal appear on the screen.
  7. Press the *Meas* button to activate the automatic measurement functions of the oscilloscope.
  8. Press the *Clear Meas* soft button, and then *Clear All*.
  9. Set *Source* to channel 1 and *Type* to *Peak-Peak*. Press *Add Measurement*. The peak-to-peak value of channel 1 should now be displayed on the screen.
  10. Write the peak-to-peak value indicated by the oscilloscope for all the following configurations of the channel.
    - a.  $2\ \mu\text{s}/\text{div}$  and  $10\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - b.  $500\ \text{ns}/\text{div}$  and  $10\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - c.  $200\ \text{ns}/\text{div}$  and  $10\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - d.  $2\ \mu\text{s}/\text{div}$  and  $1\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - e.  $2\ \mu\text{s}/\text{div}$  and  $20\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - f.  $2\ \mu\text{s}/\text{div}$  and  $100\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
    - g.  $2\ \mu\text{s}/\text{div}$  and  $500\ \text{mV}/\text{div}$ .  $V_{pp} = \underline{\hspace{2cm}}$
  11. The automatic measurement is most precise when \_\_\_\_\_
-

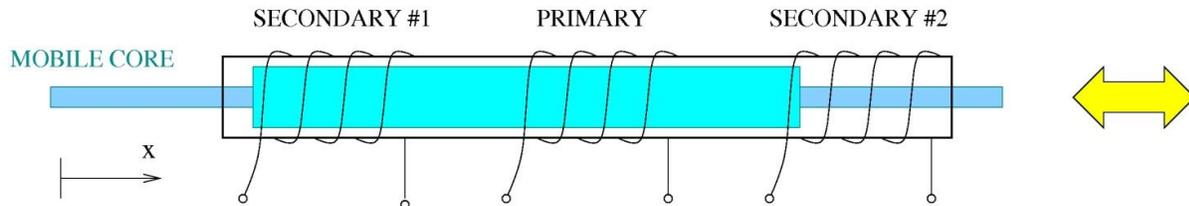12. Multimeters perform very precise AC measurements of low frequency signals. Their precision is not as good at higher frequencies, such as 100 kHz.
13. Measure the rms voltage of the waveform generator with a DMM. \_\_\_\_\_
14. Convert the DMM measurement to a peak-to-peak value:  $V_{pp} =$  \_\_\_\_\_
15. Compare the result to the value measured using the oscilloscope cursor functions. \_\_\_\_\_
16. Identify the primary and secondary windings of the LVDT.



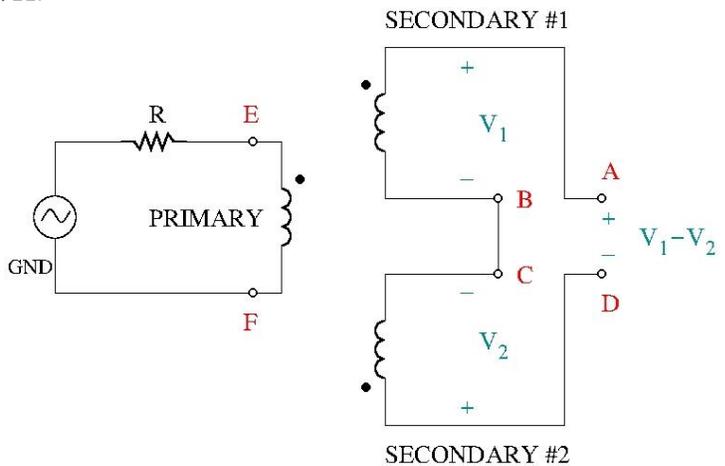17. Set the waveform generator for maximum output voltage.
18. Connect the circuit shown in the figure. Use  $R = 47\Omega$ .
19. Depending on how you have connected the secondary coils, the voltages  $V_1$  and  $V_2$  should be either in phase or  $180^\circ$  out of phase.
20. Visualize  $V_1$  on channel 1 and  $V_2$  on channel 2 when the LVDT core is in the middle.
21. If  $V_1$  and  $V_2$  are  $180^\circ$  out of phase, reconnect the secondary coils so that  $V_1$  and  $V_2$  are in phase.
22. Visualize the voltage between E and F on channel 1, and the voltage between A and D on channel 2.
23. Let  $x$  denote the displacement of the core with respect to the center position.
24. If everything is correct, the voltage between A and D should be zero when the core is in the middle position. If this does not happen, go back to step 21.
25. Measure the phase angle difference of the voltage between E and F (the primary voltage) and the voltage between A and D (the output voltage).



- When  $x < 0$ , the phase difference is \_\_\_\_\_. When  $x > 0$ , the phase difference is \_\_\_\_\_.
26. In the following steps, you will record data in Excel. Open Excel.
  27. Measure the peak-to-peak voltage between A and D for displacements of  $-1''$ ,  $-0.5''$ ,  $0''$ ,  $0.5''$ , and  $1''$  and record in a table in Excel. Label the table and indicate all units.
  28. Note that the primary voltage is not a constant, as the inductance of the primary depends on the position of the core. To obtain a more linear dependence between voltage and displacement, the primary voltage  $V_{EF}$  has to be accounted for.
  29. In this exercise the operating curve of the LVDT will be obtained. Let  $V_{1p-p}$  denote the peak-to-peak voltage of secondary 1 and  $V_{2p-p}$  the peak-to-peak voltage of secondary 2.
    - a. Measure  $V_{EF}$ ,  $V_{1p-p}$  and  $V_{2p-p}$  for 10 negative values of  $x$ , 10 positive values of  $x$ , and for  $x = 0$ .
    - b. Use a DMM for  $V_{EF}$  and the two oscilloscope channels for  $V_1$  and  $V_2$ .
    - c. Use the *measurement* functions of the oscilloscope to speed up data acquisition.
    - d. You may use the external trigger to ensure that the waveforms are always stable.
    - e. Record your data in a table with four columns, one column for each voltage and one column for  $x$ .
    - f. To detect when  $x = 0$ , press *Math*, then *Operator*, and then select *Subtract*. This will display the  $V_1 - V_2$  waveform. Note that  $x = 0$  when  $V_1 - V_2$  is zero. You may adjust the size of the waveform using the vertical sensitivity control located above the *Math* button, to its right.
    - g. Let  $V_{out,p-p} = V_{1p-p} - V_{2p-p}$ . Obtain the graph of  $V_{out,p-p}$  versus the displacement  $x$ .
    - h. Obtain also the graph of  $(V_1 - V_2)/V_{EF}$  versus the displacement  $x$ .

30. In this exercise the inductance of the primary will be determined.
- Using the oscilloscope, determine the peak-to-peak voltage of the resistor R. Make sure that your grounding connections are correct! Sketch the circuit of the primary and indicate below where you have connected the ground of the source and where the ground of the oscilloscope.
  - The voltage on the resistor R is  $V_R =$  \_\_\_\_\_
  - Calculate the peak-to-peak value of the current.  $I =$  \_\_\_\_\_
  - DMMs lose some of their accuracy when measuring high frequency AC signals. Measure the rms value of the current with a DMM.  $I =$  \_\_\_\_\_. Is the value reasonably close to close to the value obtained with the oscilloscope? \_\_\_\_\_
  - Given I, what voltage should be measured in order to calculate the inductance? Determine the inductance at  $x = 0$  and describe in detail your method. Make sure that the ground connections are correct!  $L =$  \_\_\_\_\_
31. In this exercise the mutual inductance between the primary and secondary coils will be determined. Note that the mutual inductance depends on the position of the core.
- The peak-to-peak secondary voltage  $V_s$  is related to the primary current I by the equation  $V_s = M \cdot \omega \cdot I$ , where M is the mutual inductance between primary and secondary.
  - You may assume that I is not changed significantly by the displacement of the core.
  - Let  $M_1$  denote the mutual inductance of the primary and secondary 1.
  - Use the data acquired at step 28 to obtain a table describing the dependence of  $M_1$  on x.
  - Obtain also the graph of  $M_1$  versus x.
  - Describe the method you have used to calculate  $M_1$ .
- Determine also the mutual inductance  $M_2$  of the primary and secondary 2.
  - Obtain also the graph of  $M_2$  versus x.
  - Compare the results at parts e and h and interpret them.
32. Compare your results to the ideal curve shown in Fig. 14.10 of the textbook. Explain differences.

33. How would you improve the LVDT design that you used in the lab?

34. (Optional) In this exercise the coupling coefficient will be determined. The coupling coefficient between the primary and secondary 1 has the formula  $k = \frac{M_1}{\sqrt{L_1 L}}$

- a. Determine the inductance of the secondary  $L_1$  and the inductance of the primary  $L$  at  $x = -1''$ ,  $-0.5''$ ,  $0.5''$ , and  $1''$ .
- b. Determine the coupling coefficient. Record the results in your spreadsheet.