



# Connecting Electric Circuits. Digital Multimeters. Power Sources.

M.V. Iordache, *EEGR2051 Circuits and Measurements Lab*, Fall 2020, LeTourneau University  
See <https://mviordache.name/EEGR2051> for more information.

# How to Connect Electric Circuits

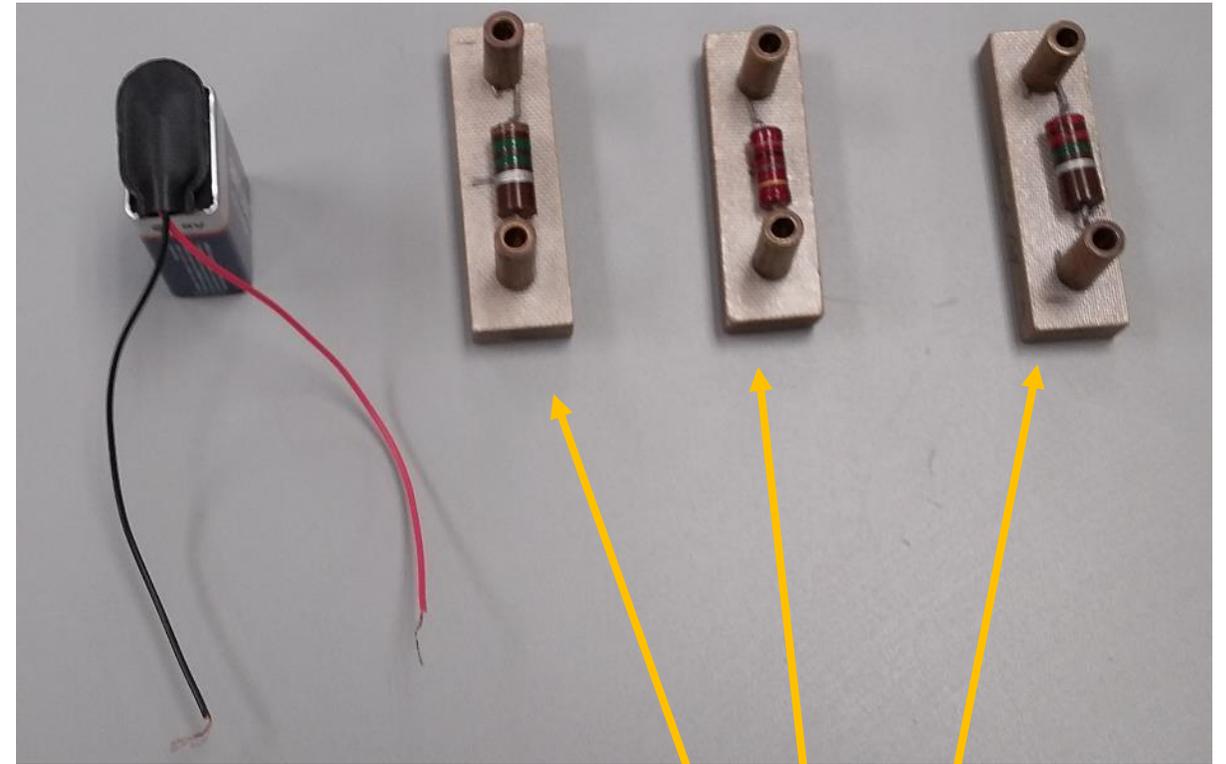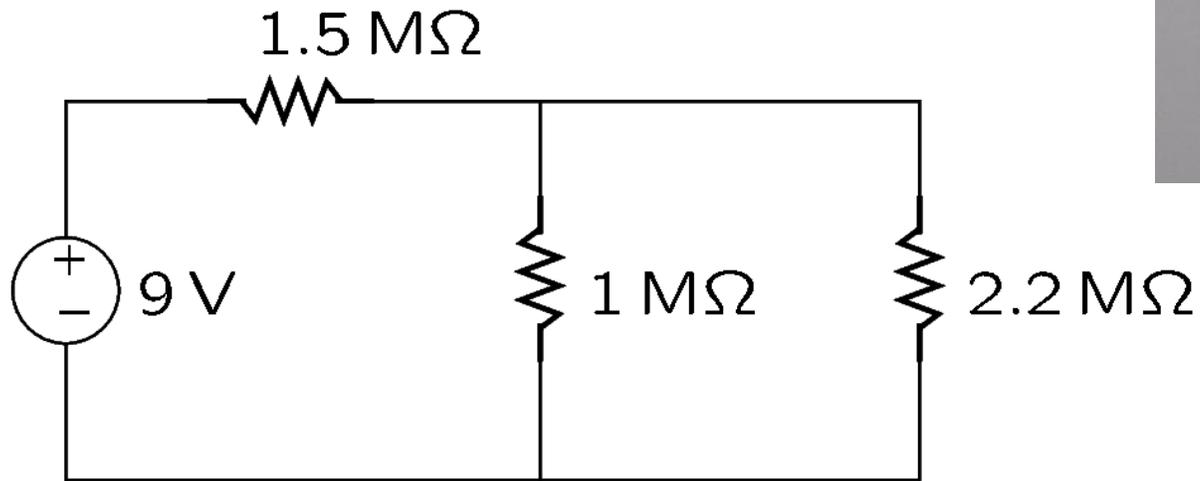
# Example

Suppose that a 9 V battery, an 1 M $\Omega$  resistor, an 1.5 M $\Omega$  resistor, and a 2.2 M $\Omega$  resistor should be connected as shown in the schematics below.




RESISTORS

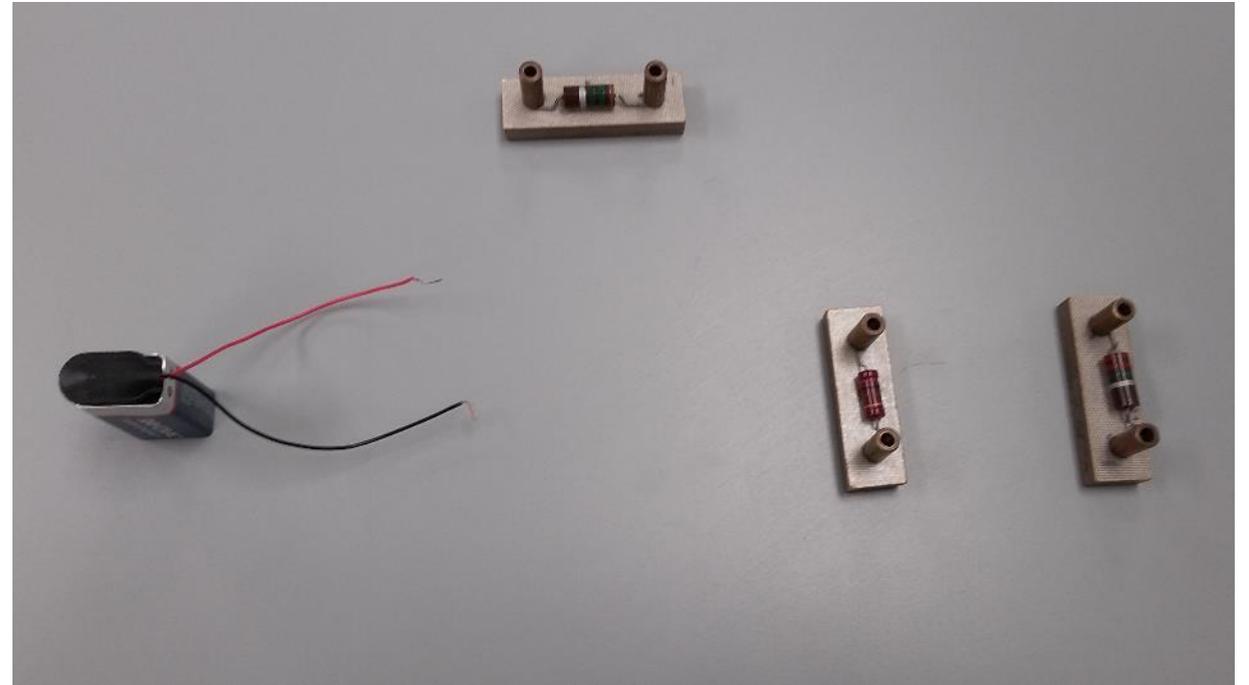*Place the components in the order shown in the schematics.*





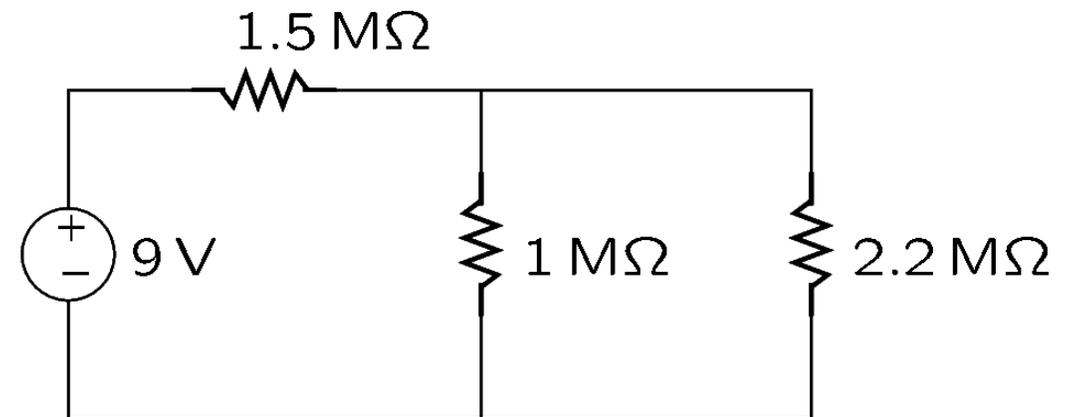*In the schematics, the lines represent cables or other conductors that should connect the components.*






*Begin making the connections shown on the schematics.*

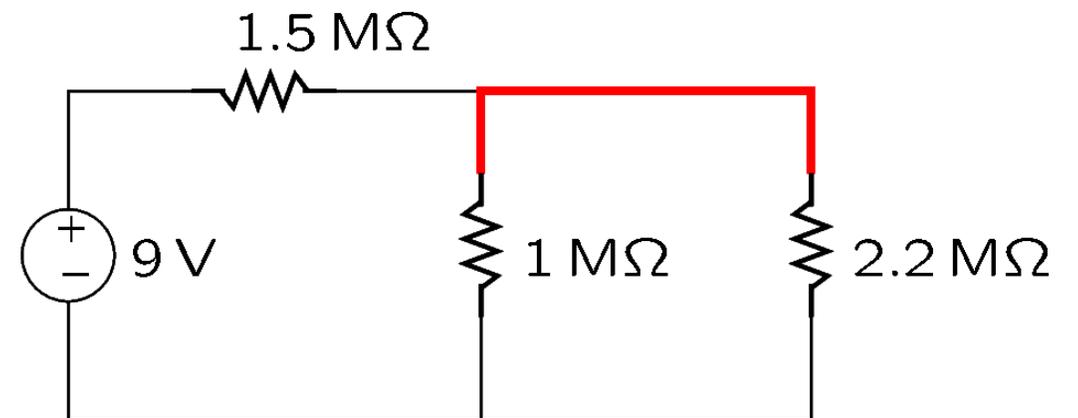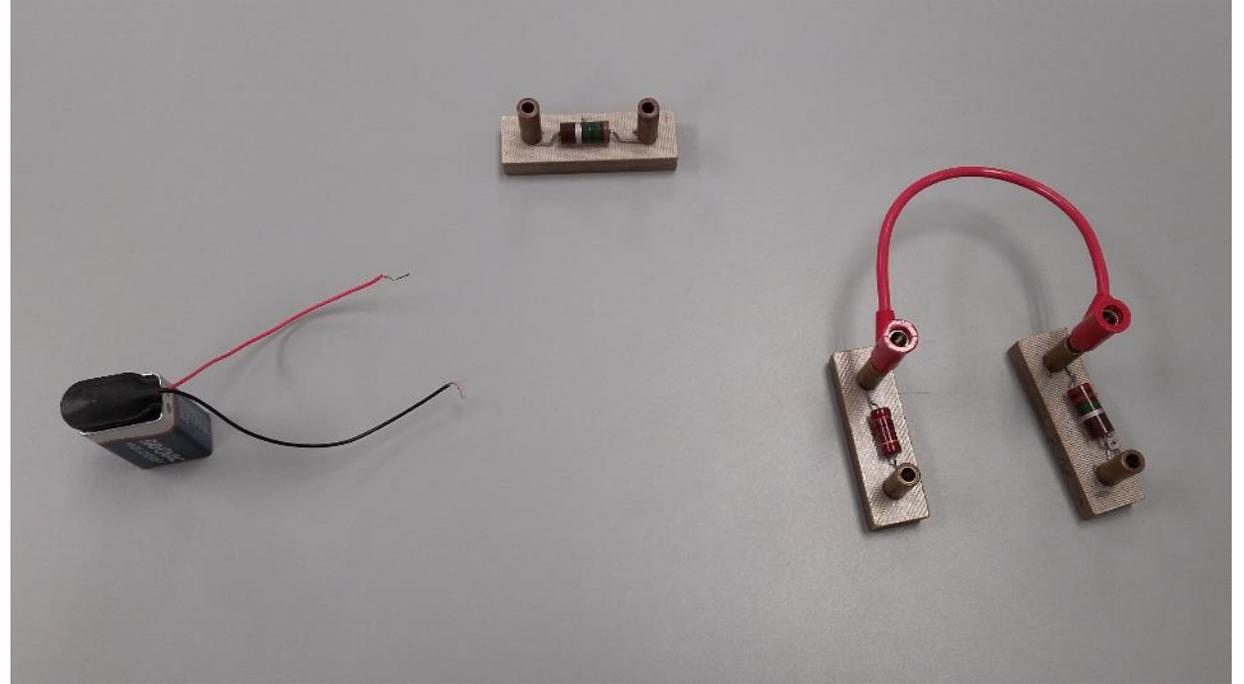*In this example, the top terminals of the  $1\text{ M}\Omega$  and  $2.2\text{ M}\Omega$  resistors were connected first.*




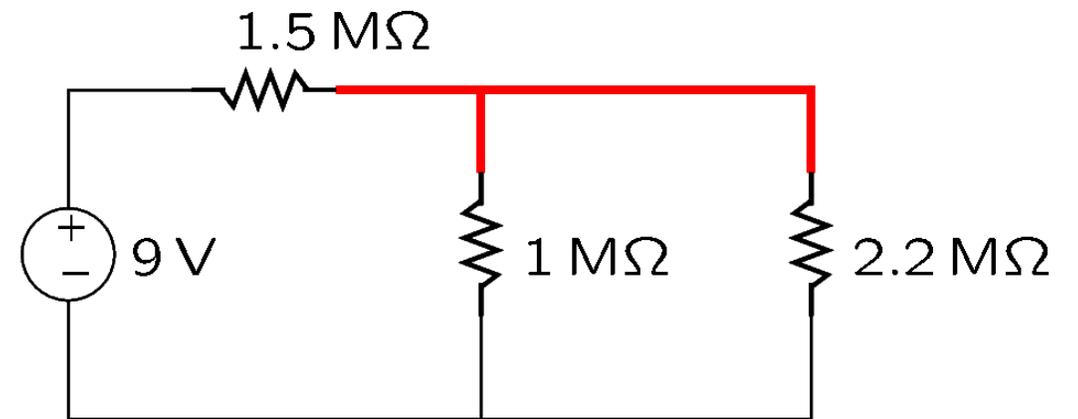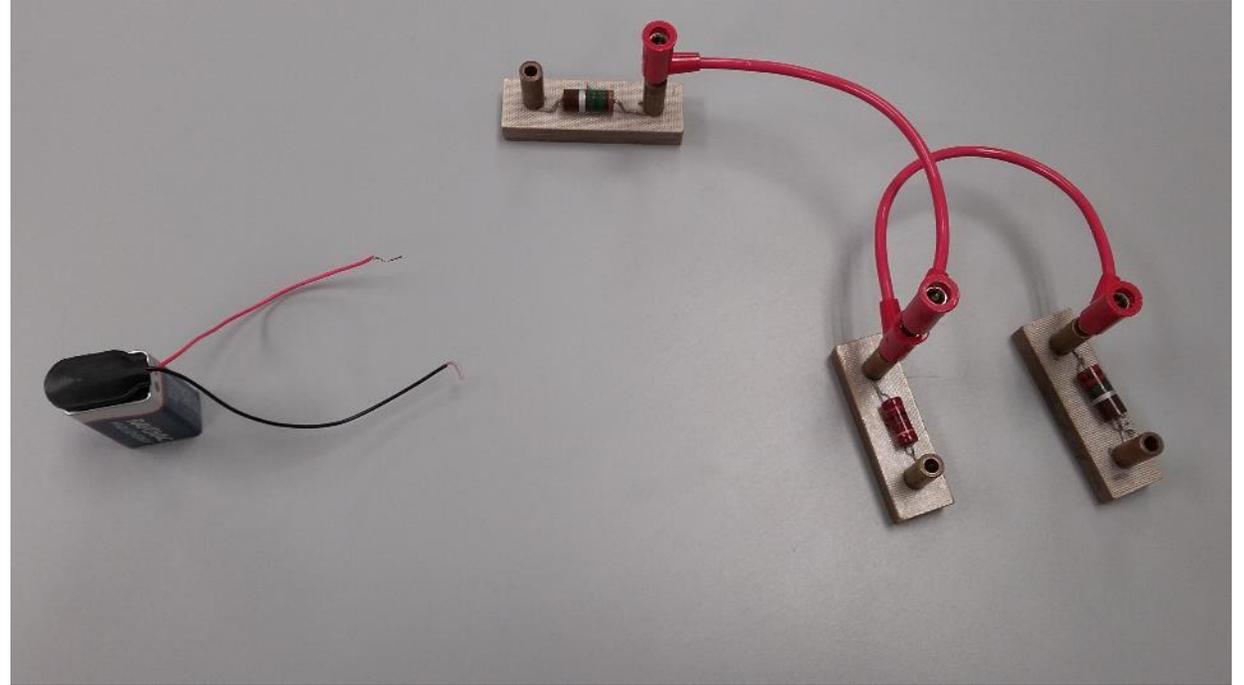
*The  $1\text{ M}\Omega$  and the  $1.5\text{ M}\Omega$  resistors were connected next.*



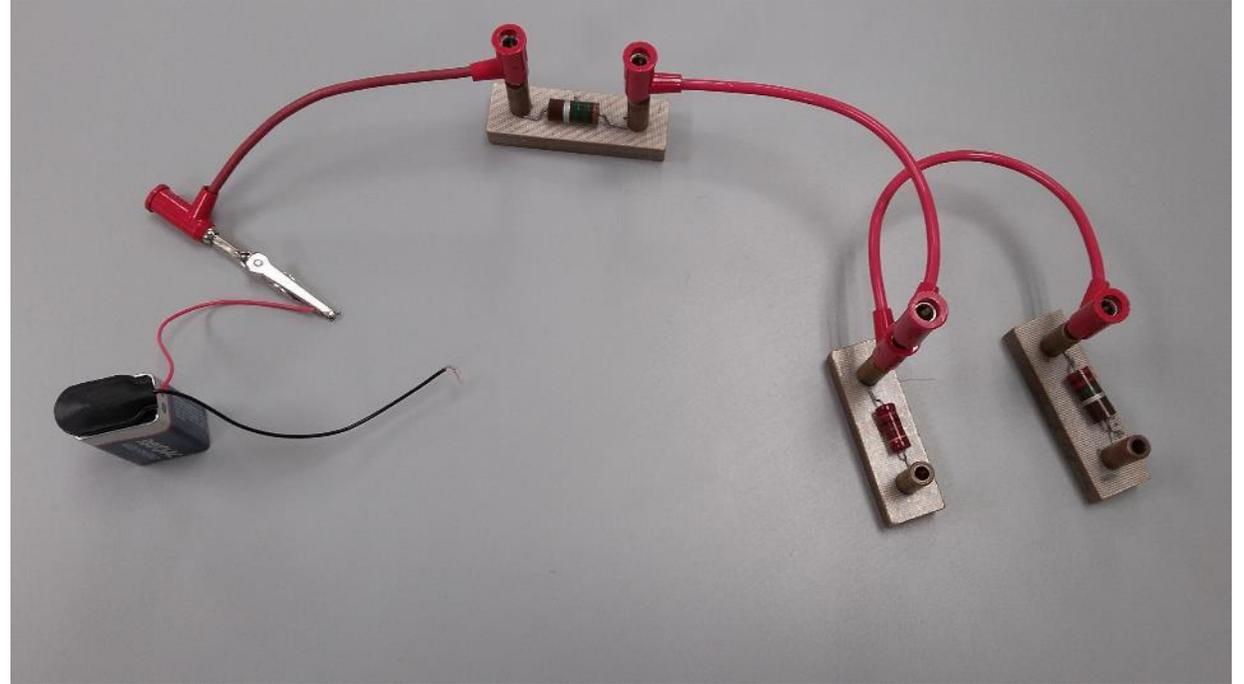


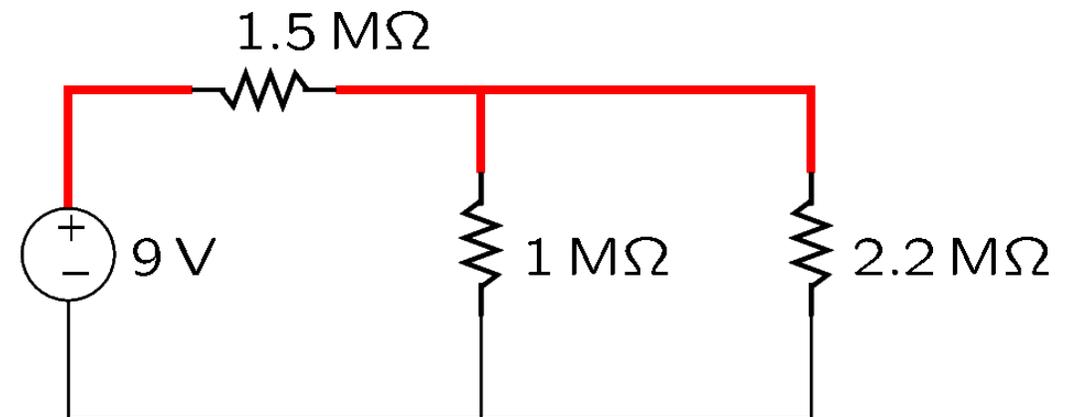*Next, the  $1.5\text{ M}\Omega$  resistor was connected to the  $+$  (red) terminal of the source.*




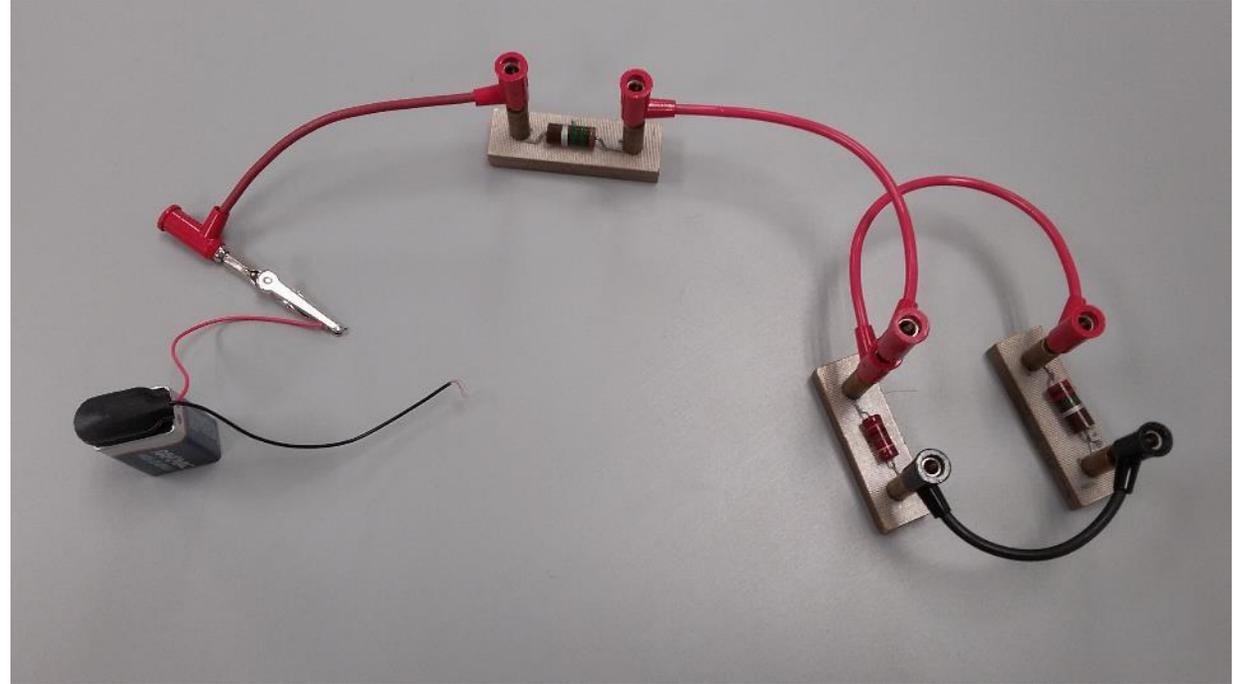


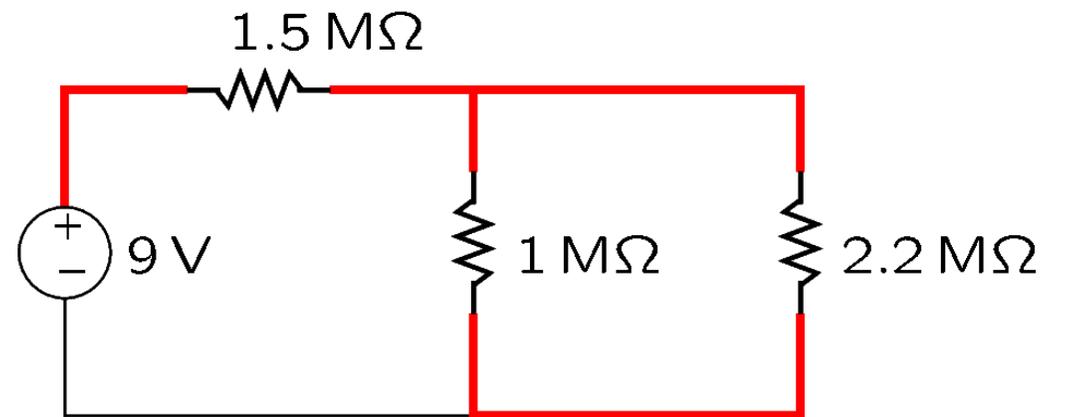*Next, the bottom terminals of the  $1\text{ M}\Omega$  and  $2.2\text{ M}\Omega$  resistors were connected.*



*Next, the  $1\text{ M}\Omega$  resistor was connected to the  $-$  (black) terminal of the battery.*



*The circuit is now complete.*

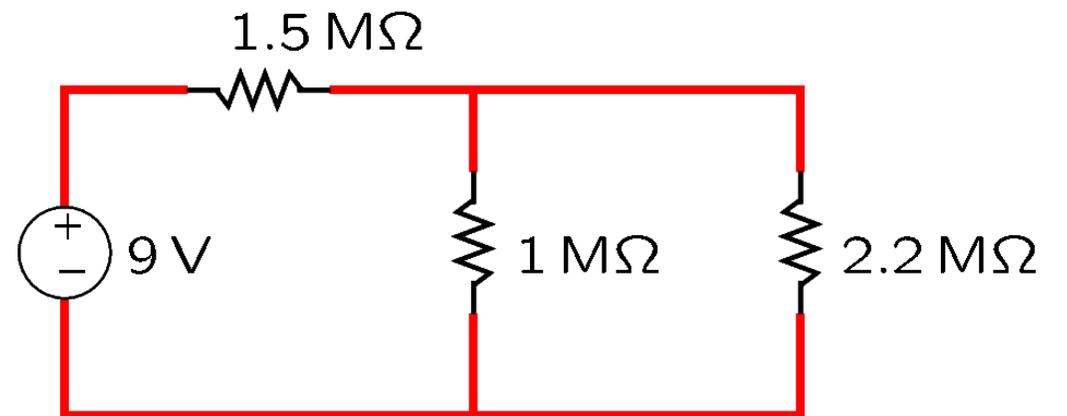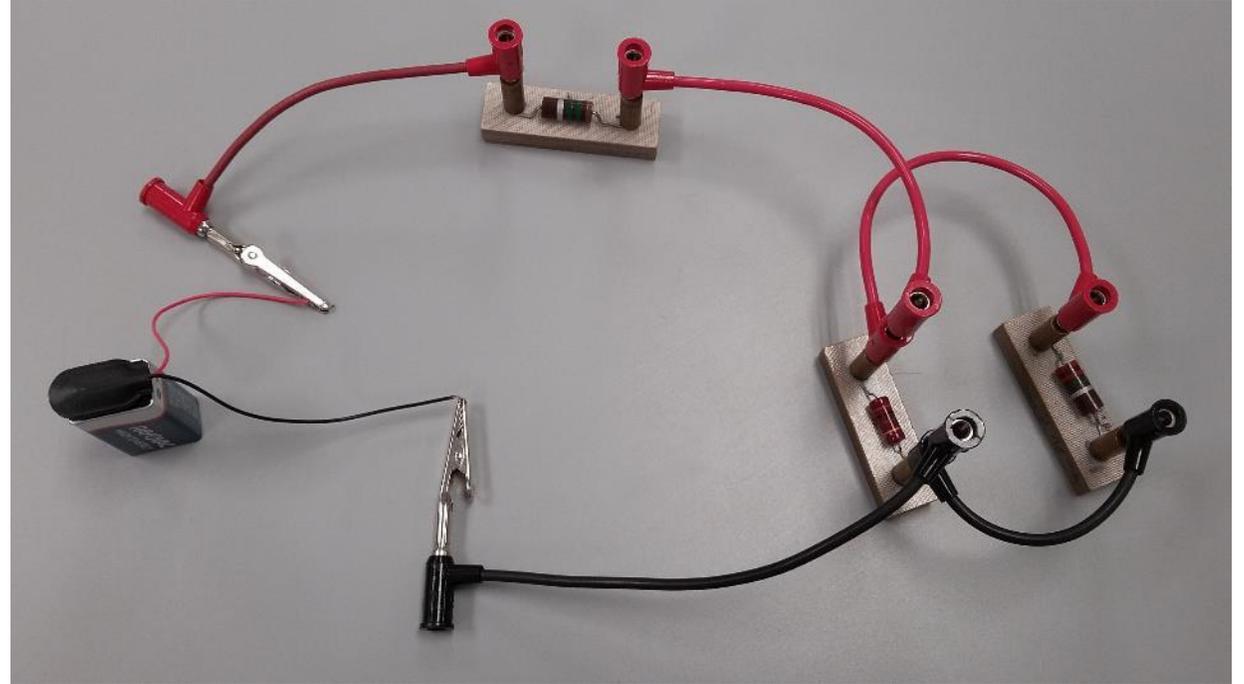

*Make all connections shown on the schematics.*

*Ensure that the circuit has no other connections besides those on the schematics.*

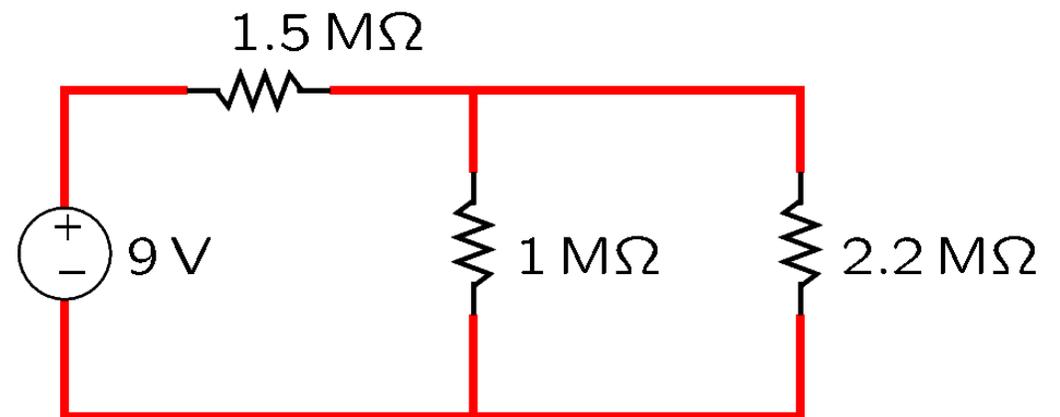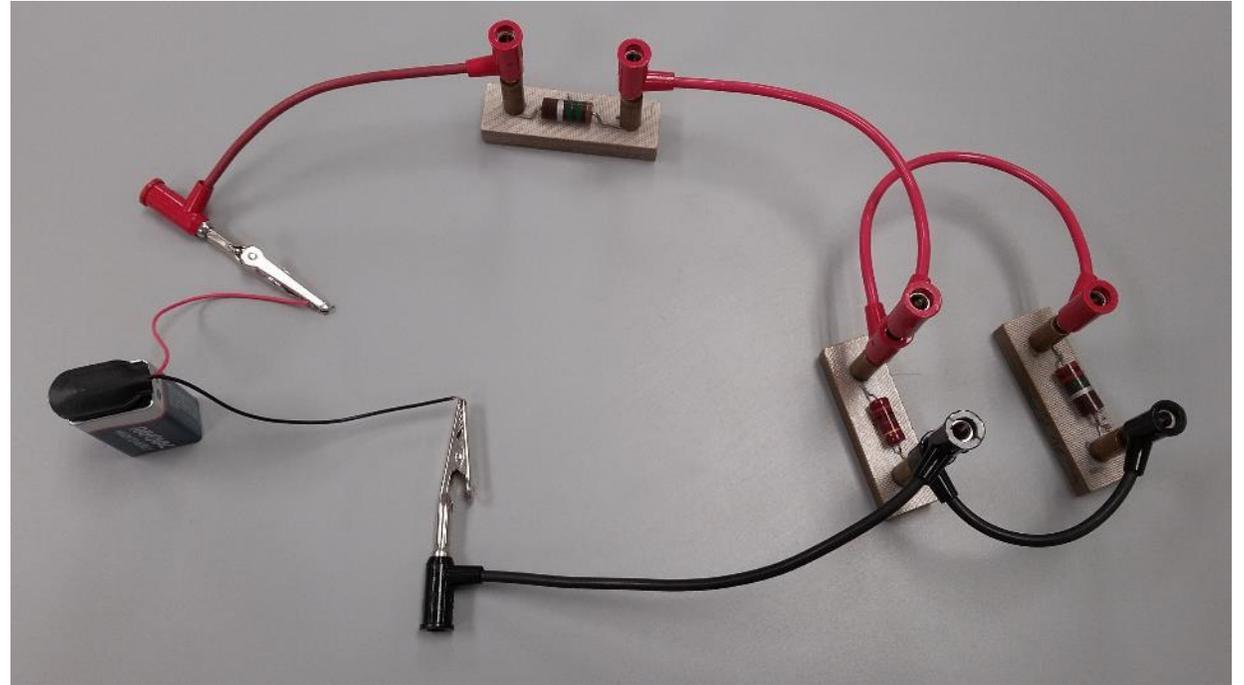*A circuit will be easier to debug if you use black cables for connections to the minus terminal of the source and **red** cables for all other connections.*




# Digital Multimeters

# Digital Multimeters (DMMs)

- A **voltmeter** measures Volts (voltage).
- An **ammeter** measures Amperes (current).
- An **ohmmeter** measures Ohms (resistance).
- A DMM can be operated either as a voltmeter, or as an ammeter, or as an ohmmeter.

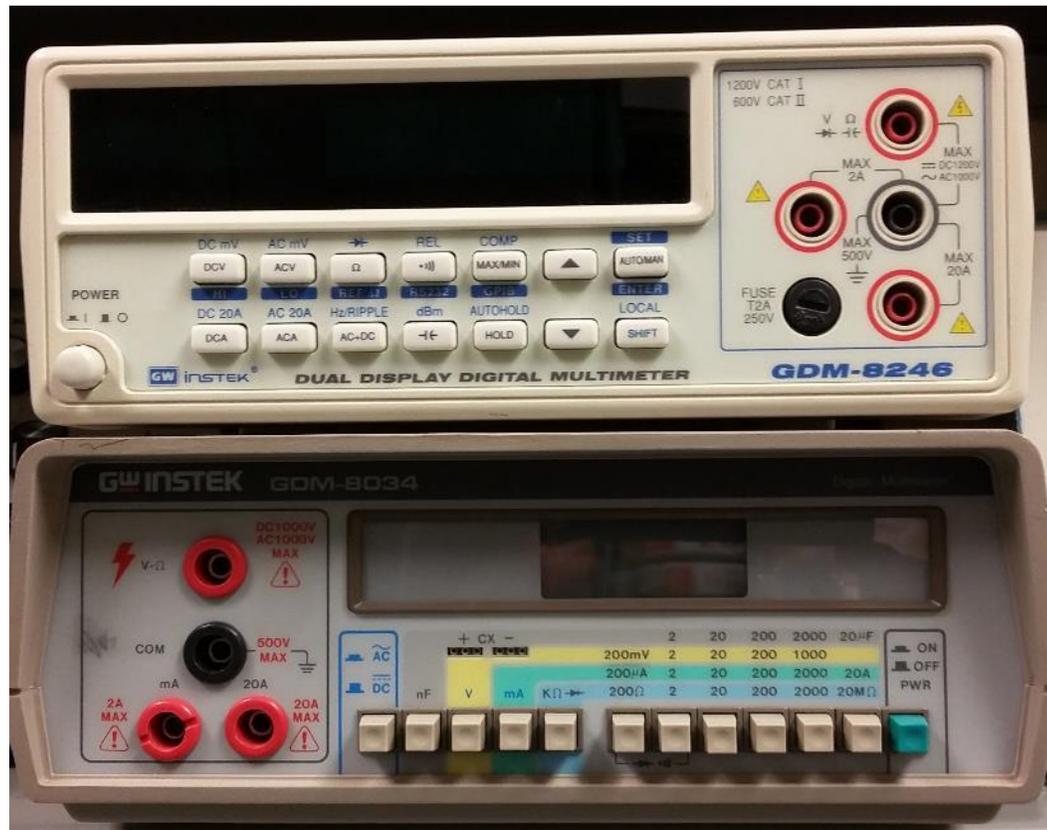
# Benchtop DMMs

- Are usually powered from the wall outlet.



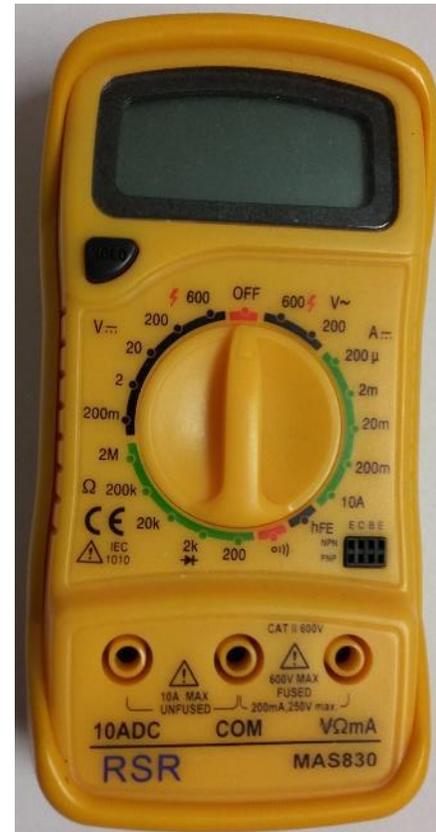
# Handheld DMMs

- Are battery powered.
- They are usually less precise than benchtop DMMs.



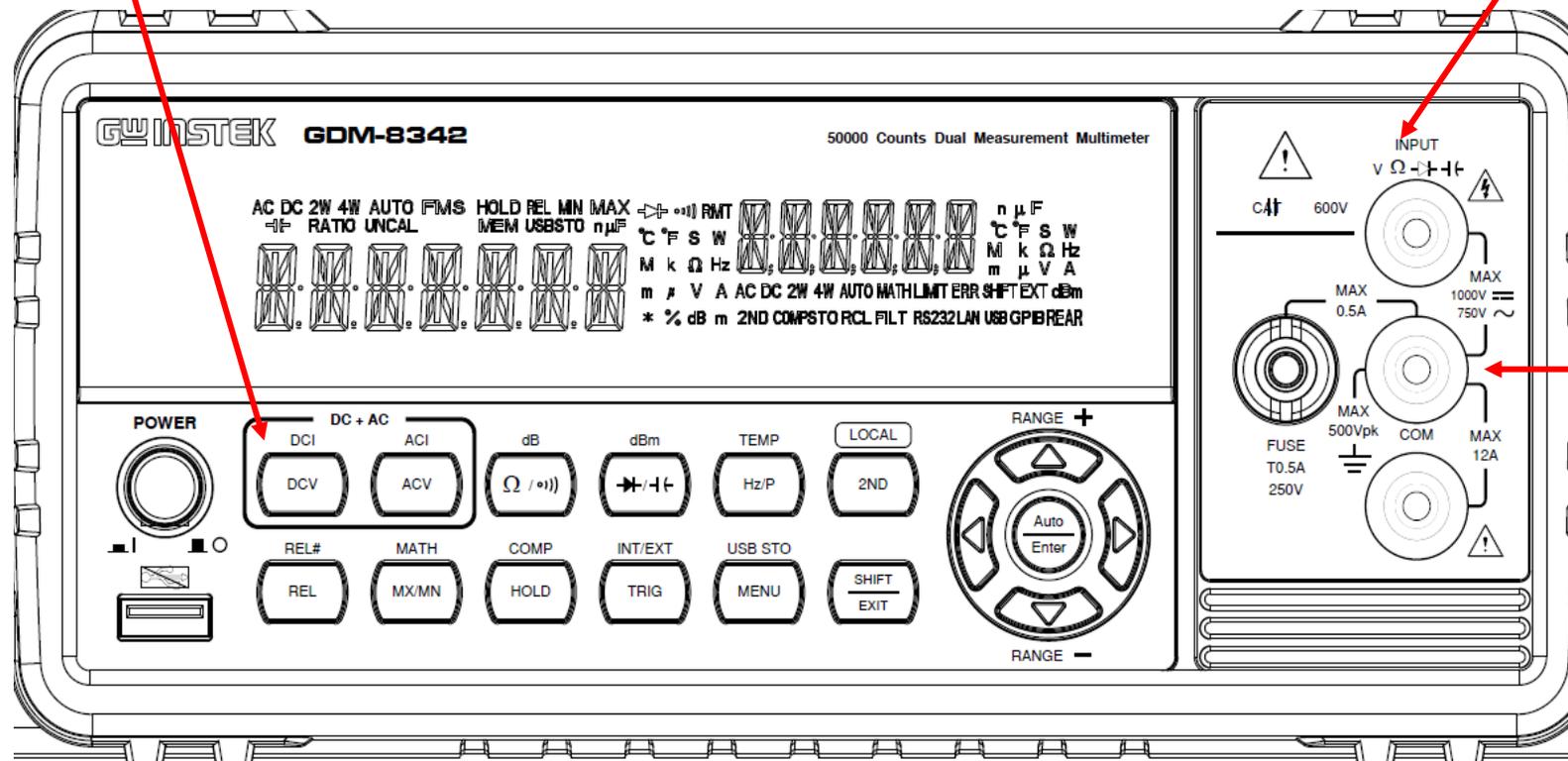
# Digital Multimeters—Example

- To measure **voltage** with the multimeter shown below:
  - Press DCV to measure DC Volts.
  - Measure the unknown voltage using the terminals marked with V and COM.



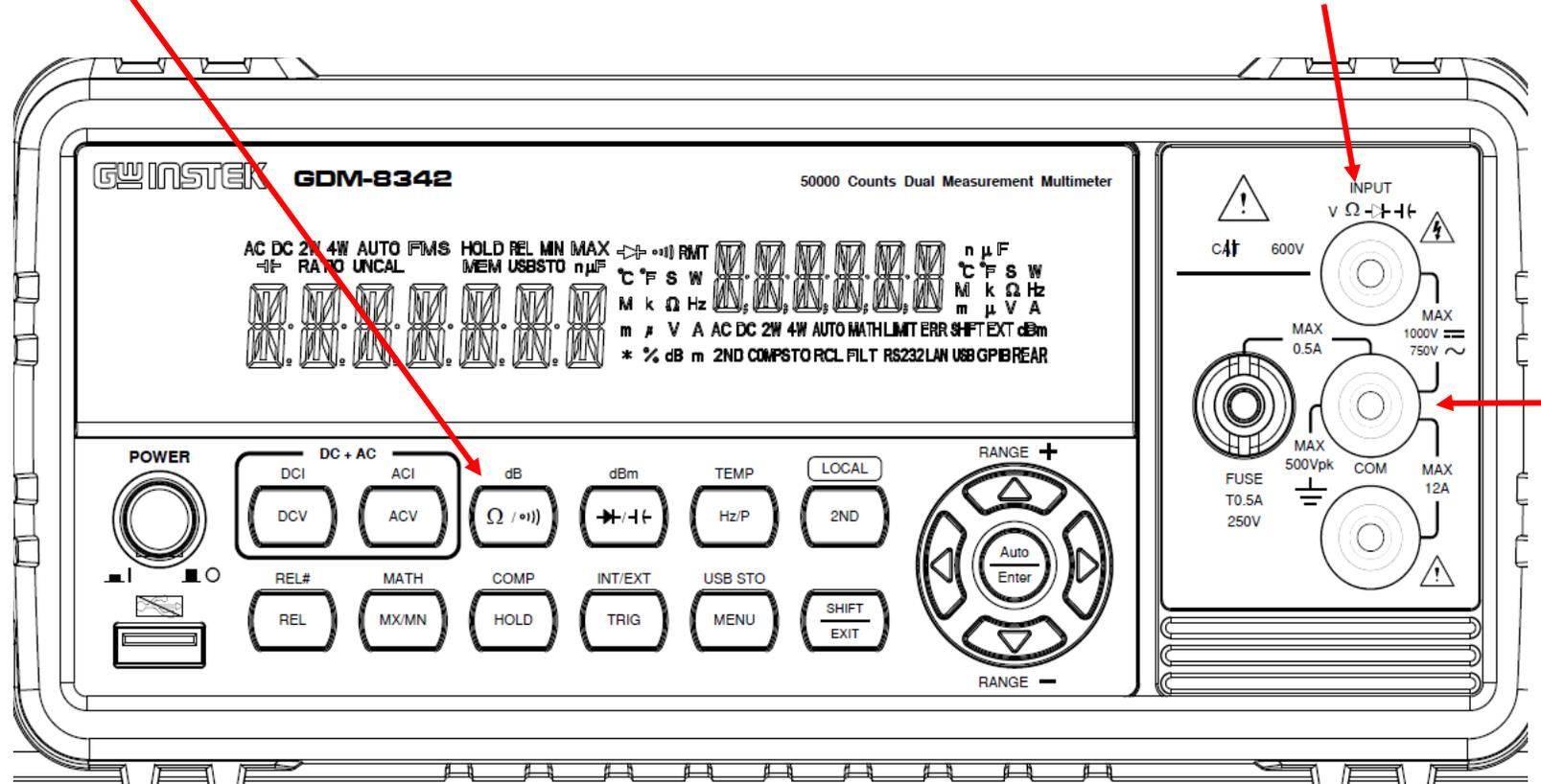
# Digital Multimeters—Example

- To measure **resistance**:
  - Press  $\Omega$  to measure ohms.
  - Measure the resistance using the terminals marked with  $\Omega$  and COM.



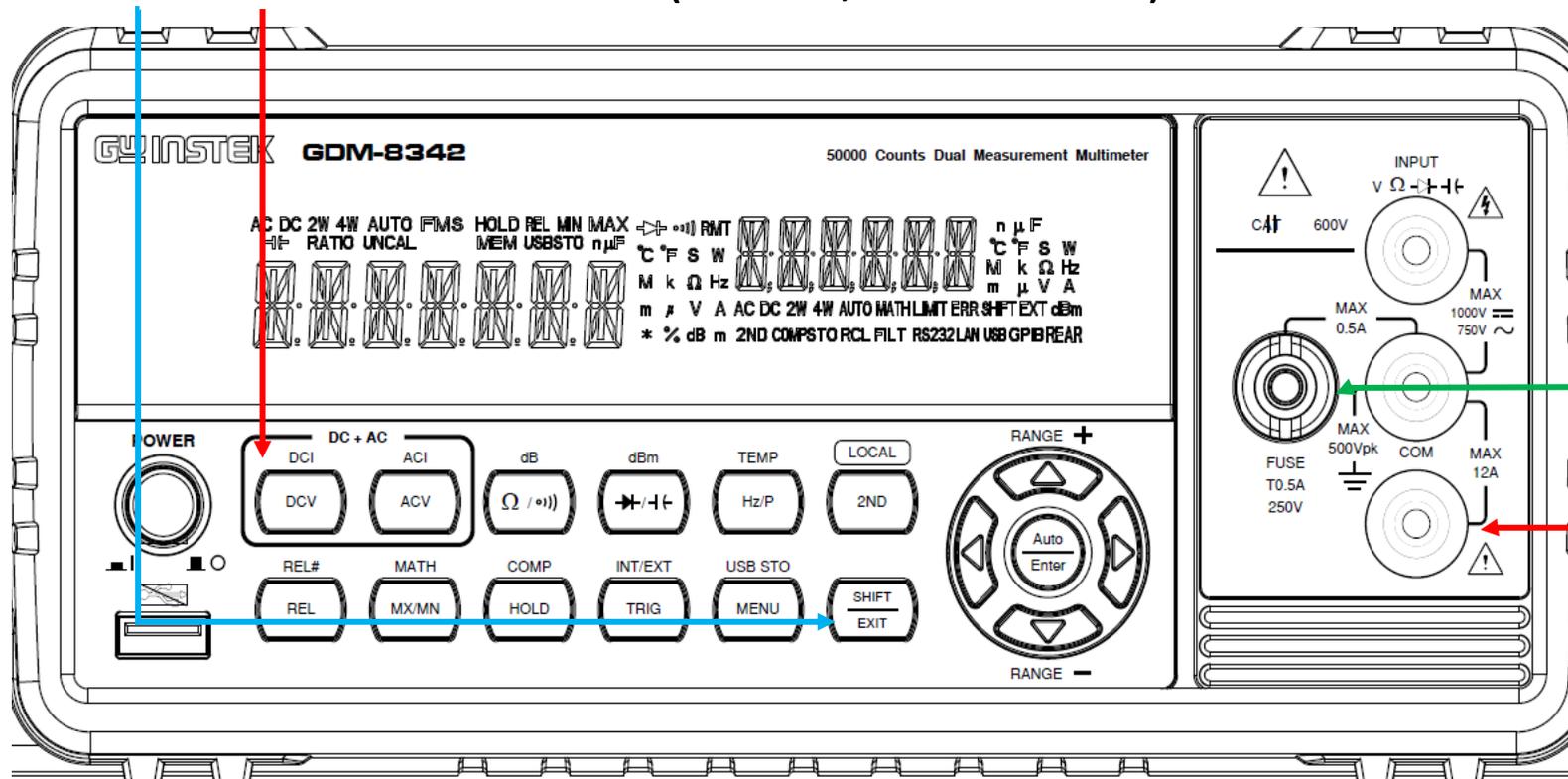
# Digital Multimeters—Example

- To measure current:
  - For currents below 12 A, use the COM terminal and the **high current terminal**.
  - For currents below 0.5 A, use the COM terminal and the **low current terminal**.
  - Press Shift + DCV to select DCI (that is, DC current).


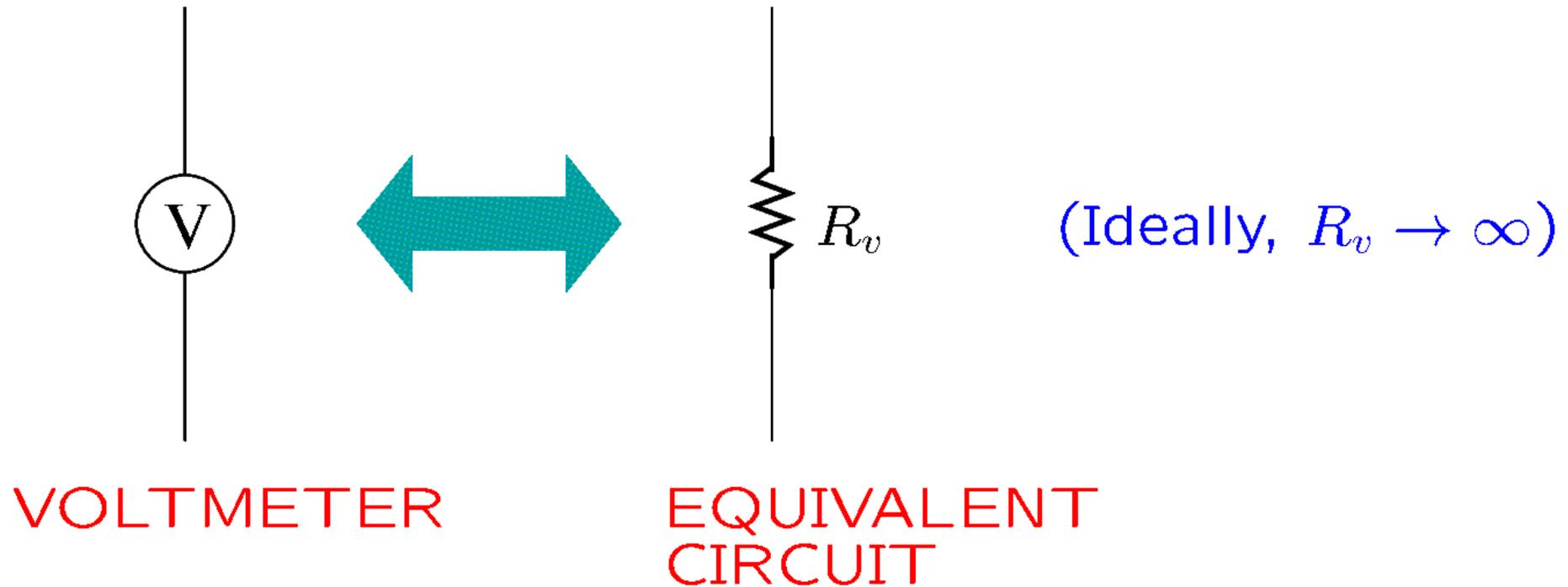
# Voltmeters



- A voltmeter is equivalent to a resistor of very high value (ideally,  $\infty$ ).



# Voltmeters


- The voltage of a component is measured by connecting the voltmeter across the component.

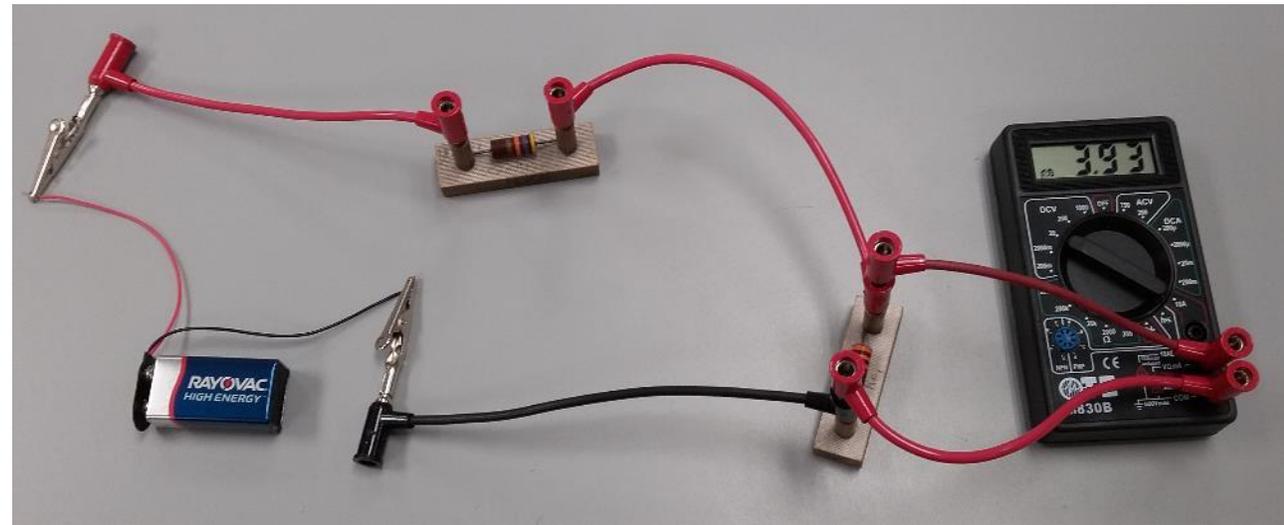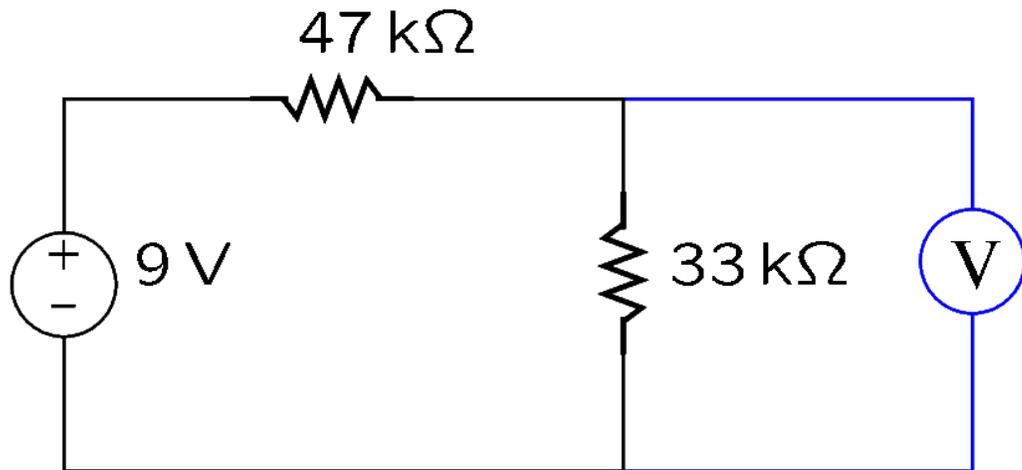*Example: The DMM was connected as in the figure to measure the voltage of the 33 k $\Omega$  resistor.*


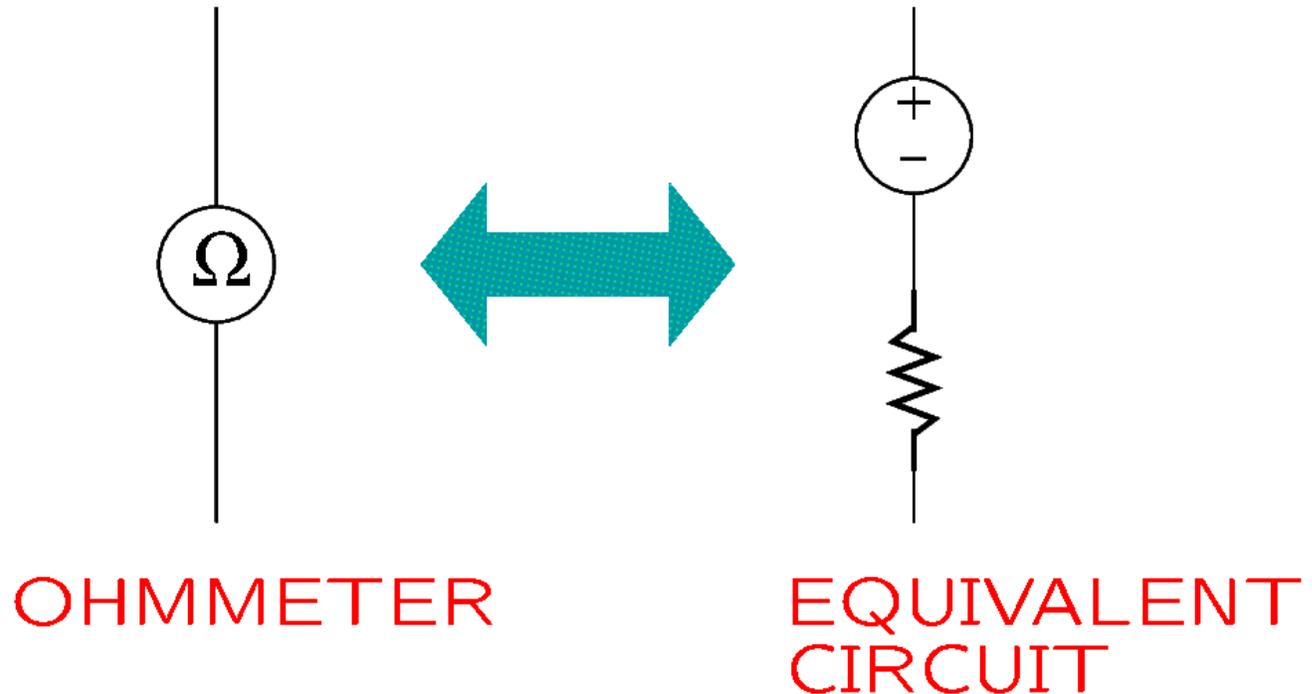
# Ohmmeters



- An ohmmeter is equivalent to a resistor in series with a source of voltage.
- An ohmmeter applies voltage to create a current and determine the unknown resistance value.



# Ohmmeters

- To measure the resistance of a component:
  1. **Disconnect** first the component from the circuit.
  2. Connect the component to the ohmmeter.

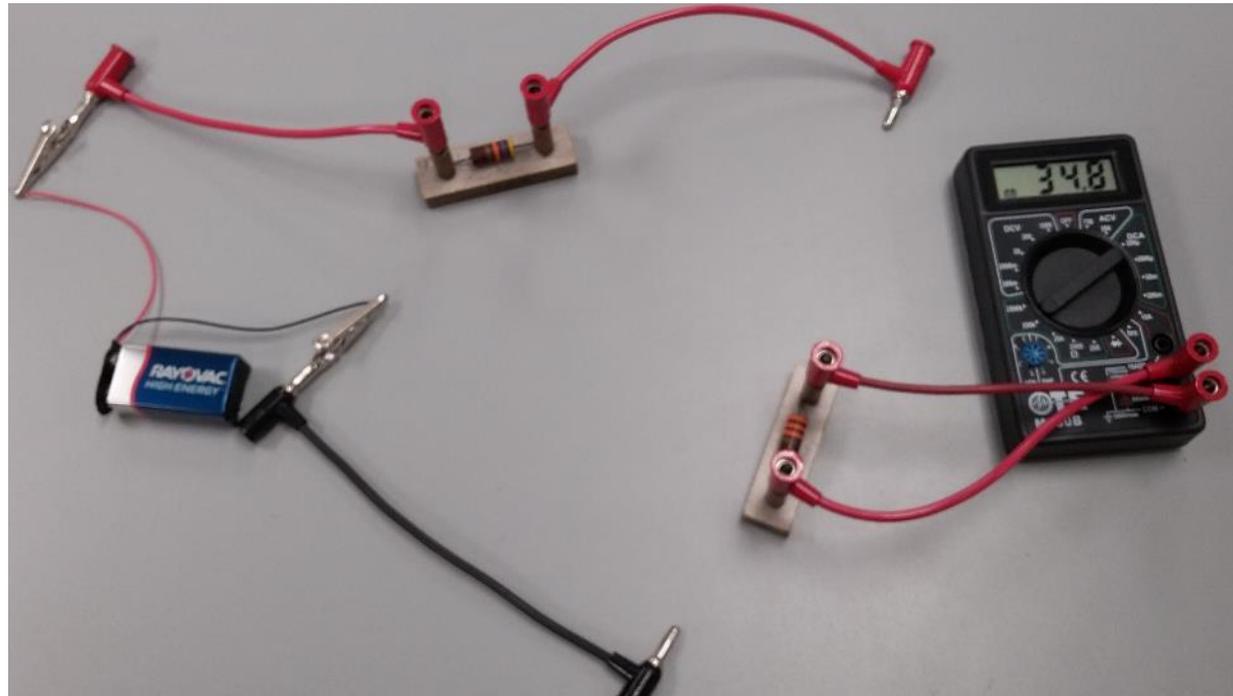
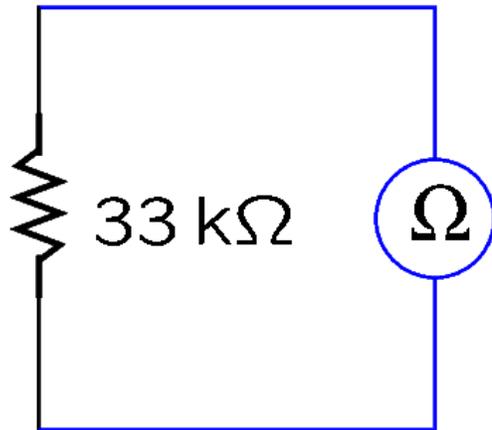
*Example: The DMM was connected as in the figure to measure the exact value of the 33 k $\Omega$  resistor. The result was 34.8 k $\Omega$ .*



# Ohmmeters


- It is essential to disconnect first the component from the circuit.
- Otherwise, the measured value will be likely incorrect.

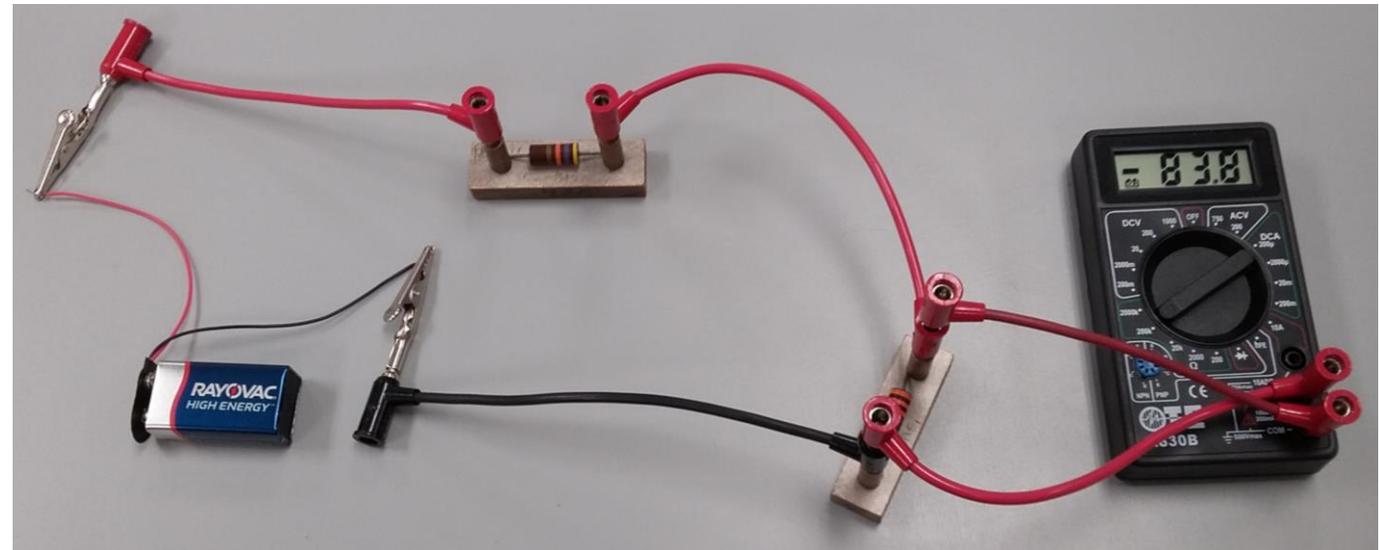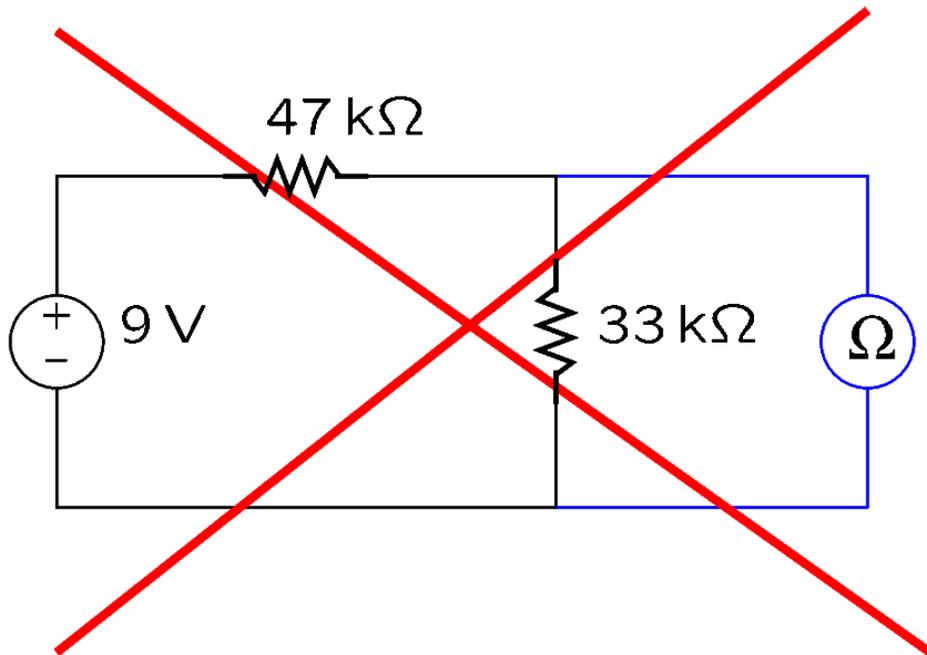*Example: The figure shows an incorrect way of measuring the 33 k $\Omega$  resistor. Note that the DMM displays –83.8 k $\Omega$ !*


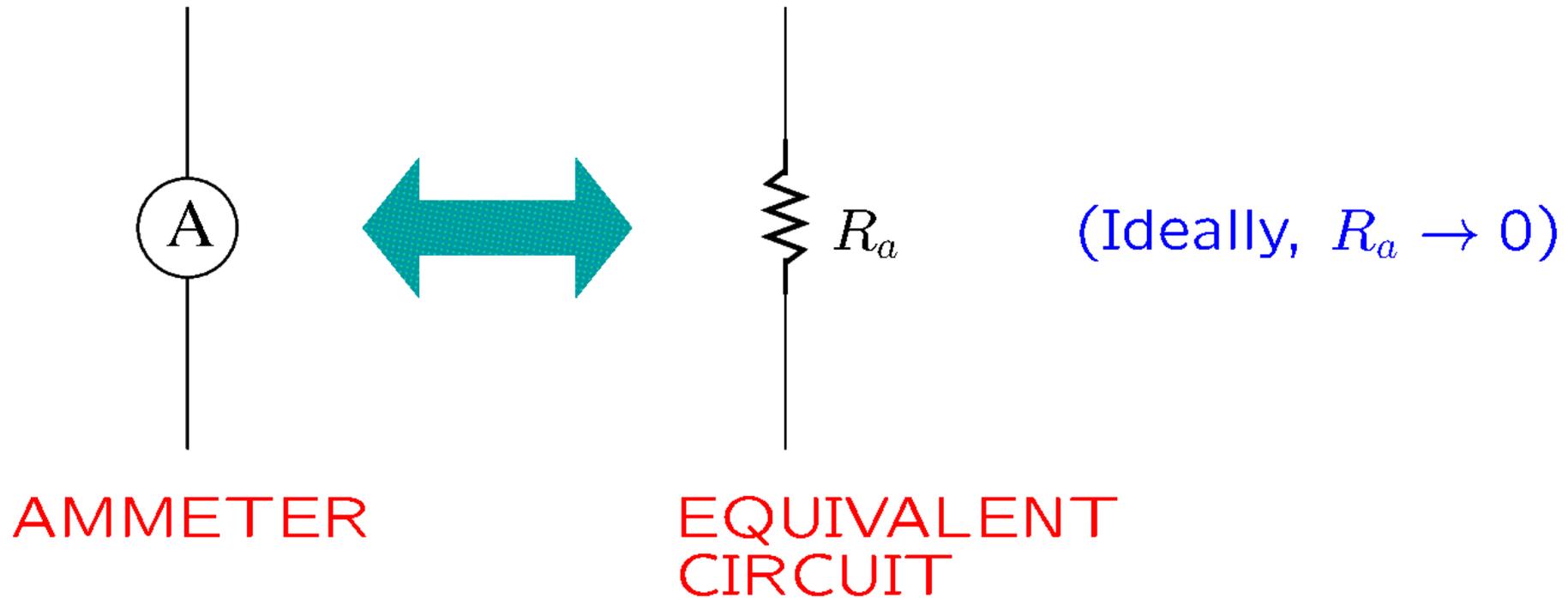
# Ammeters



- An ammeter is equivalent to a resistor of very low value (ideally, 0).



# Ammeters



- The current of a component is measured by placing the ammeter in series with the component.

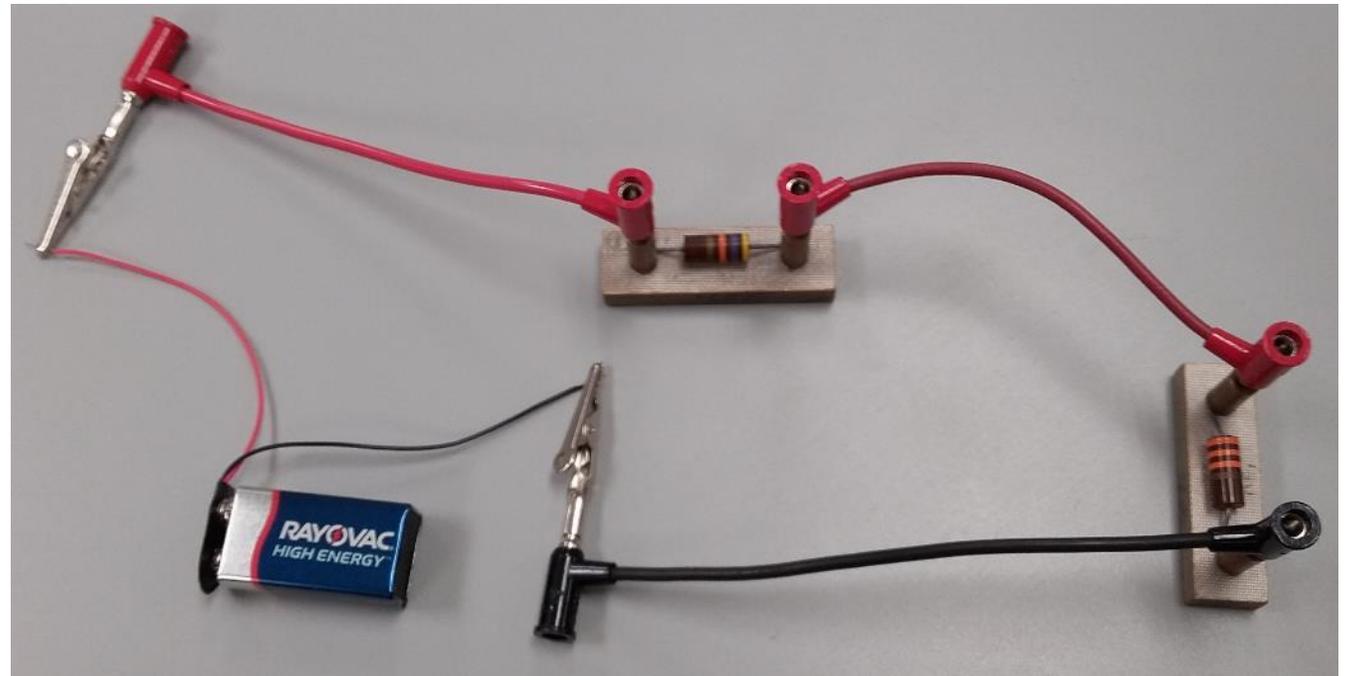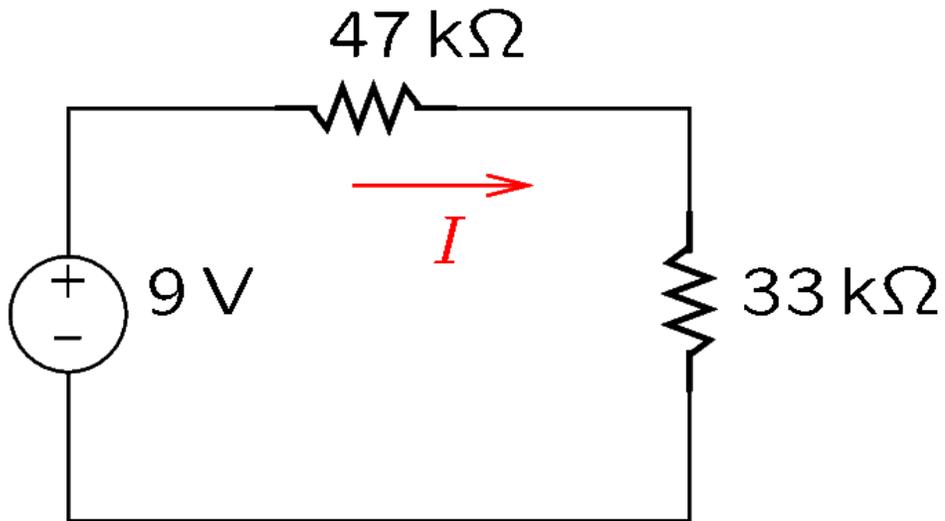*Example: The current of the 47 k $\Omega$  resistor should be measured.*


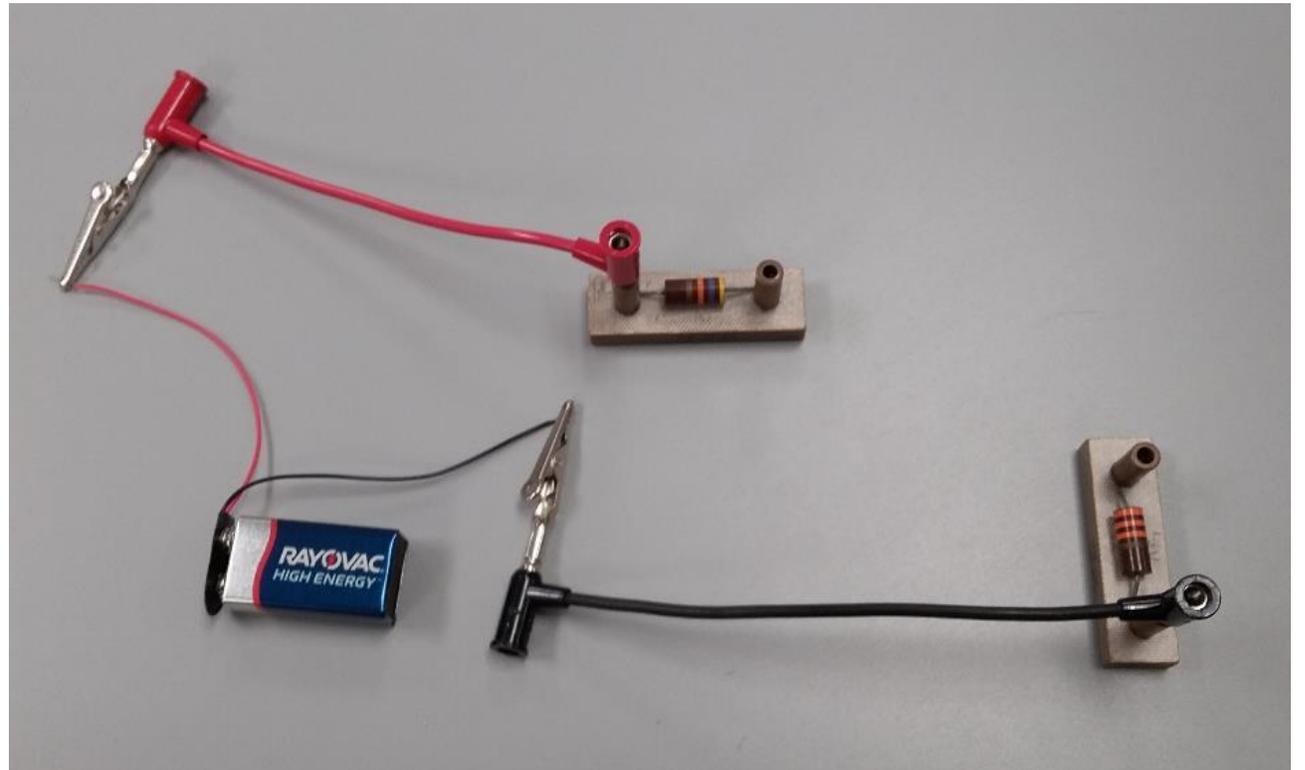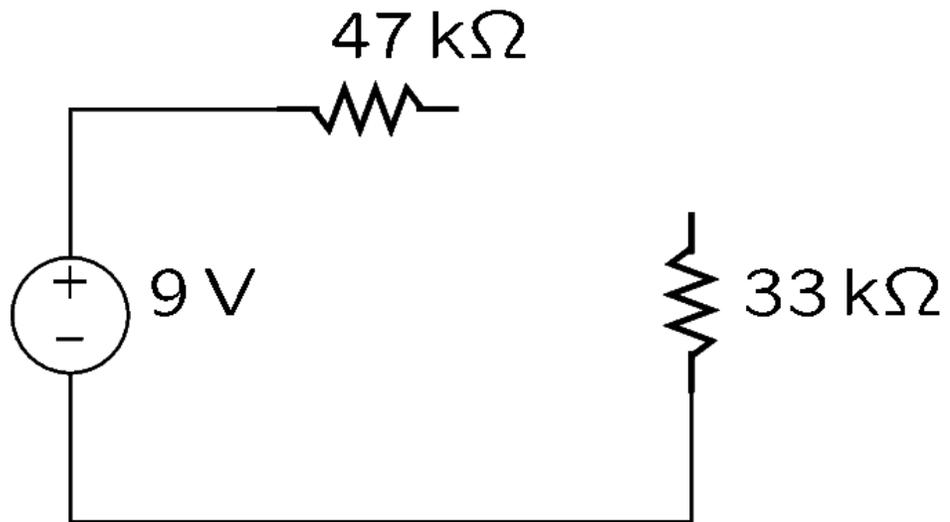
# How to Measure Current—Example (Continued)



*Step 1: Disconnect the resistor at one of its ends.*


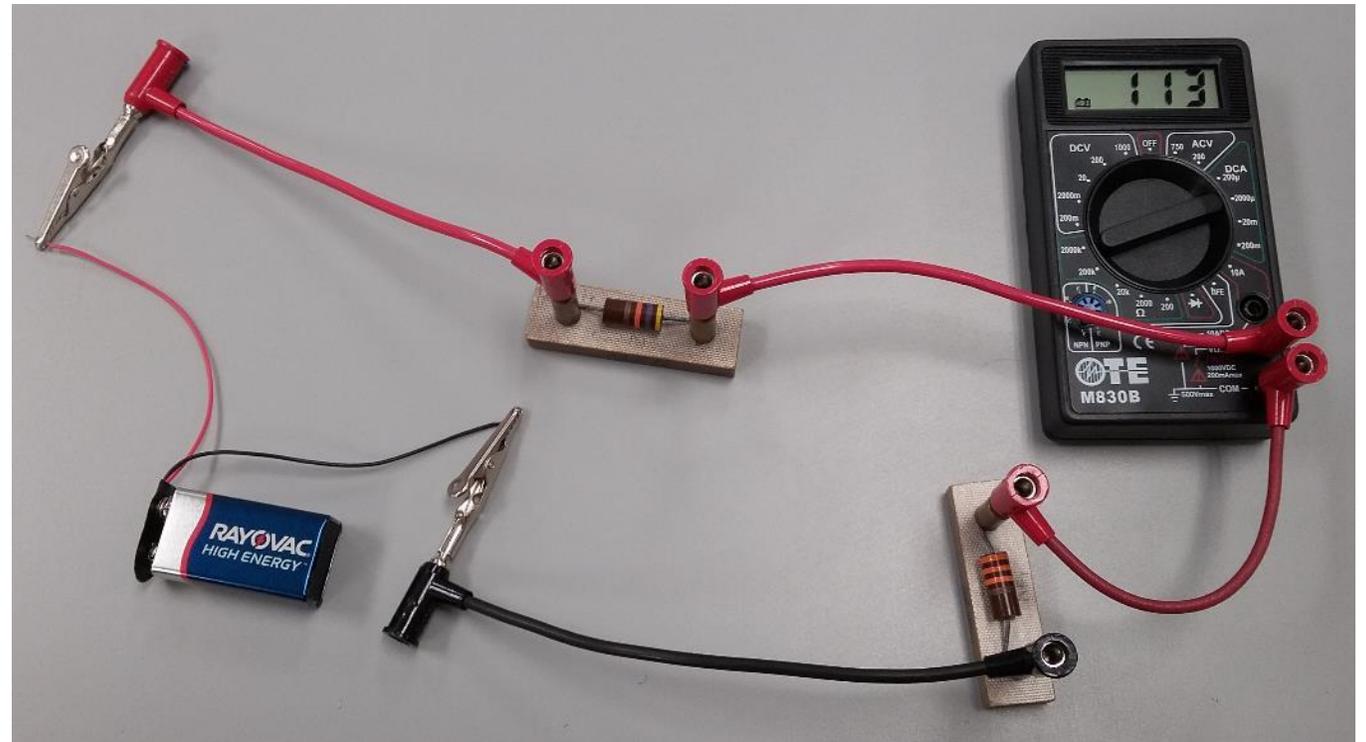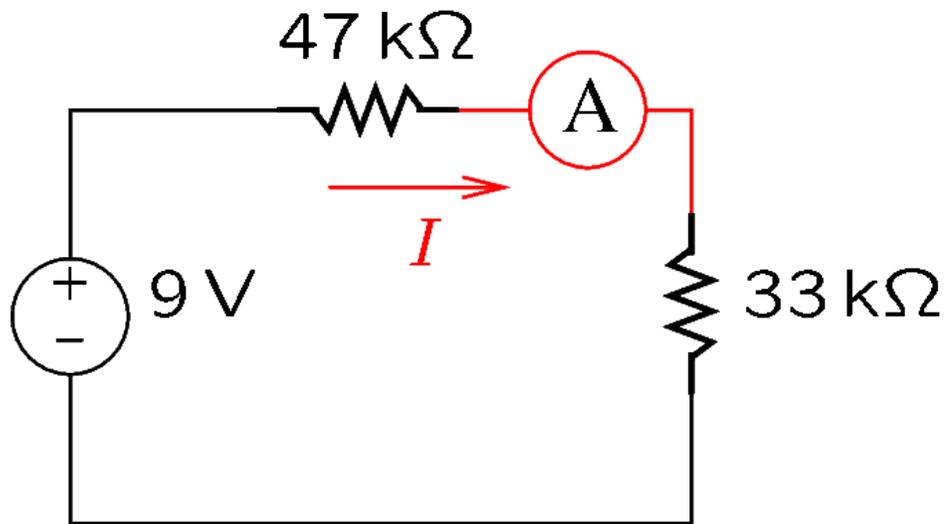
# How to Measure Current—Example (Continued)



*Step 2: Reconnect the resistor by means of an ammeter, so that the current to or from the resistor flows through the ammeter.*

*The ammeter shows a current  $I = 113 \mu\text{A}$ .*



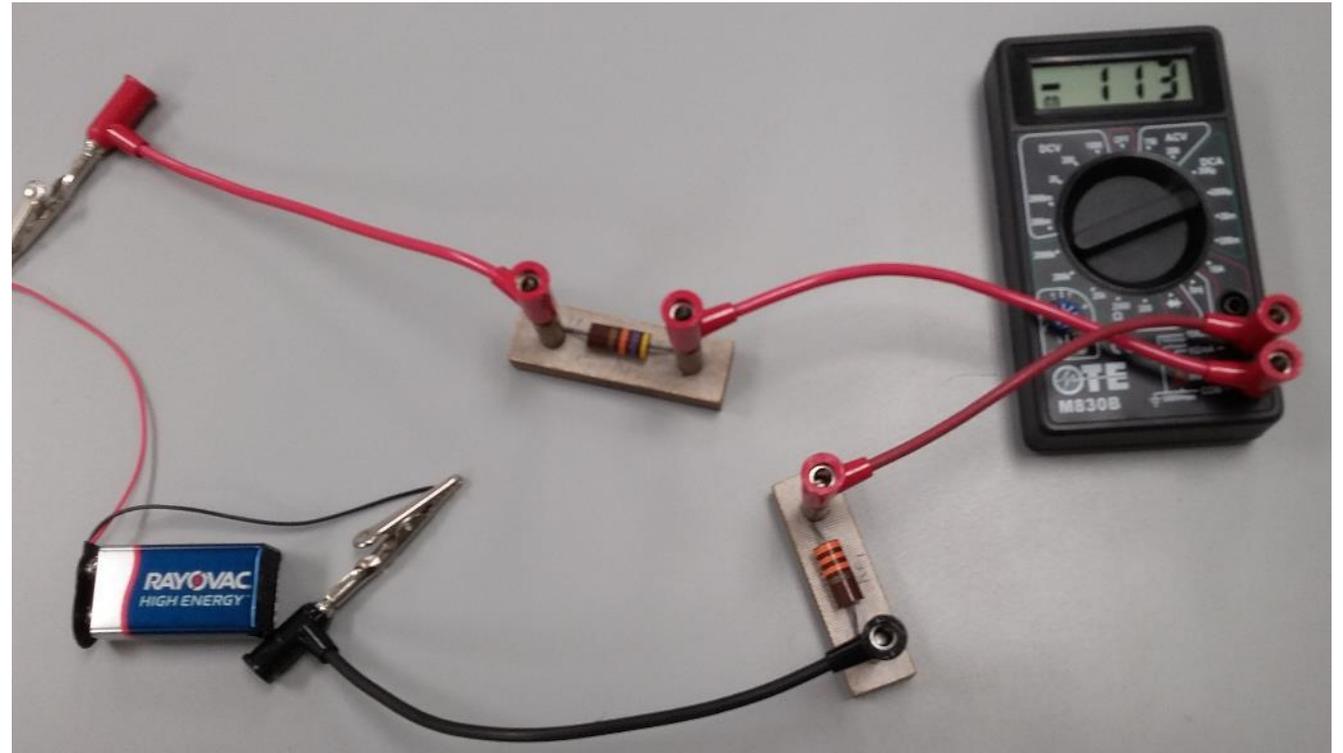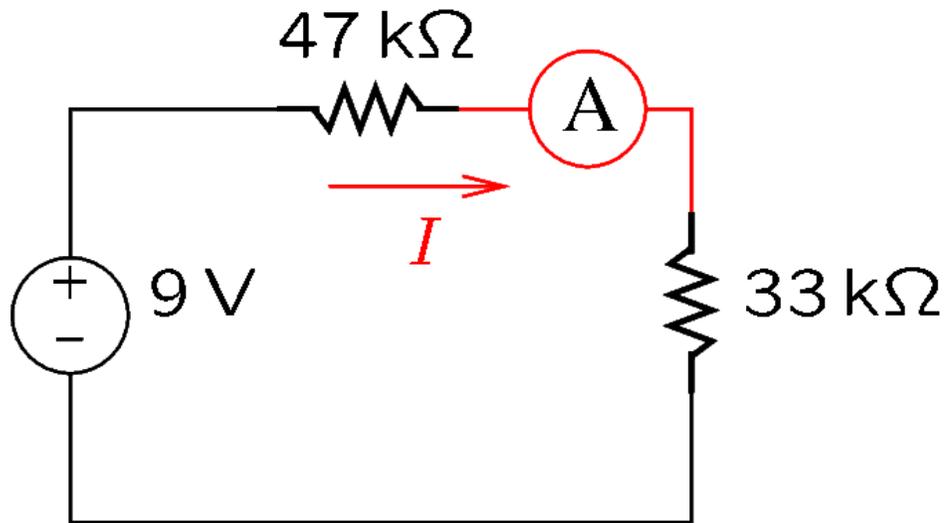
# How to Measure Current—Example (Continued)

*Note that by interchanging the connections of the ammeter, the sign of the measured current changes:  $-113 \mu\text{A}$  instead of  $+113 \mu\text{A}$ .*



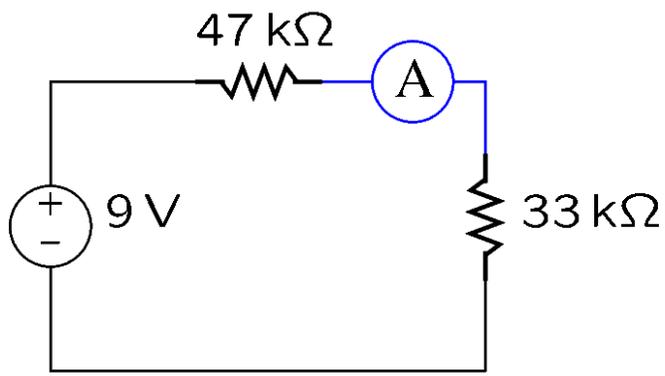
# How to Measure Current

- *Ammeters are always connected in series.*
- *An ammeter may not be connected across a component.*
- *Otherwise, the ammeter will show an incorrect value and the ammeter fuse may get blown.*
- *Note that when the fuse is blown, the ammeter indicates a zero current (since no current can flow through it).*





CORRECT

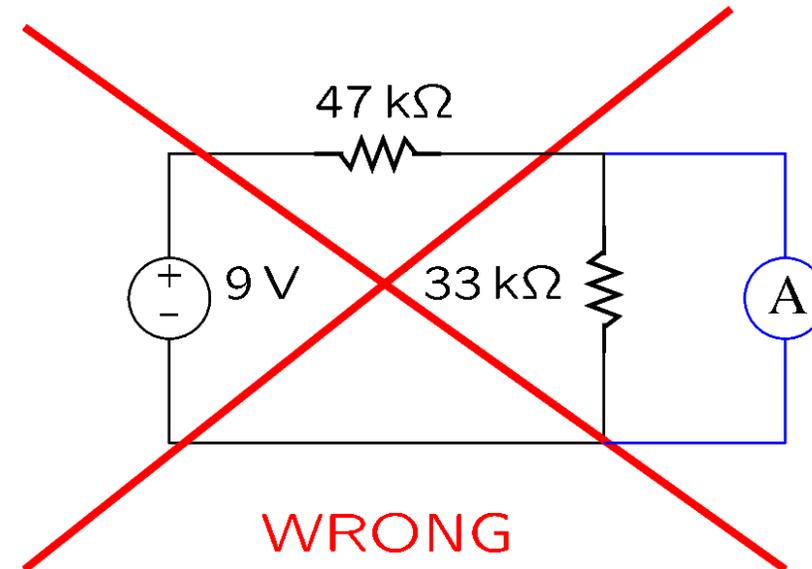

WRONG

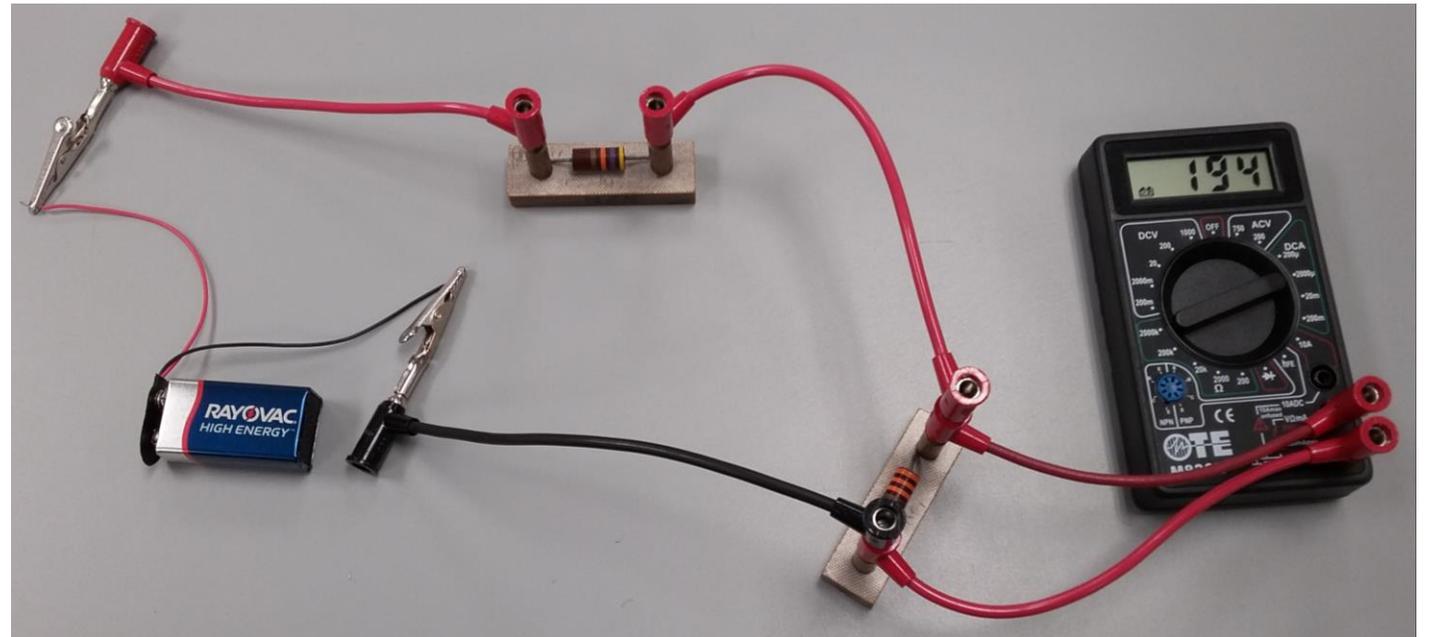
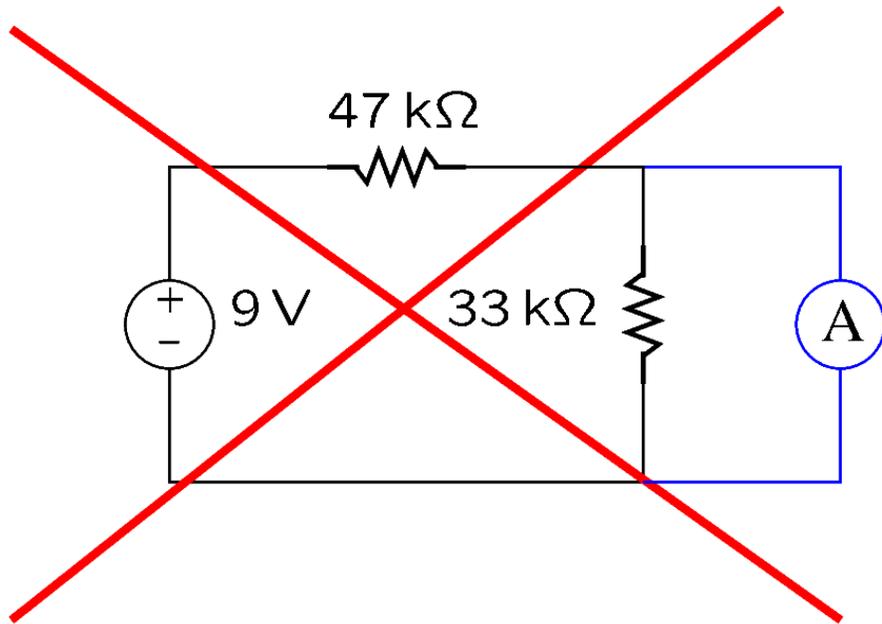
# How to Measure Current—Example (Continued)

- *In the previous example, the current of the  $33\text{ k}\Omega$  resistor was  $113\ \mu\text{A}$ .*
- *The figure below shows an incorrect way to measure this current.*
- *The measurement is wrong because the ammeter is in parallel, not in series.*



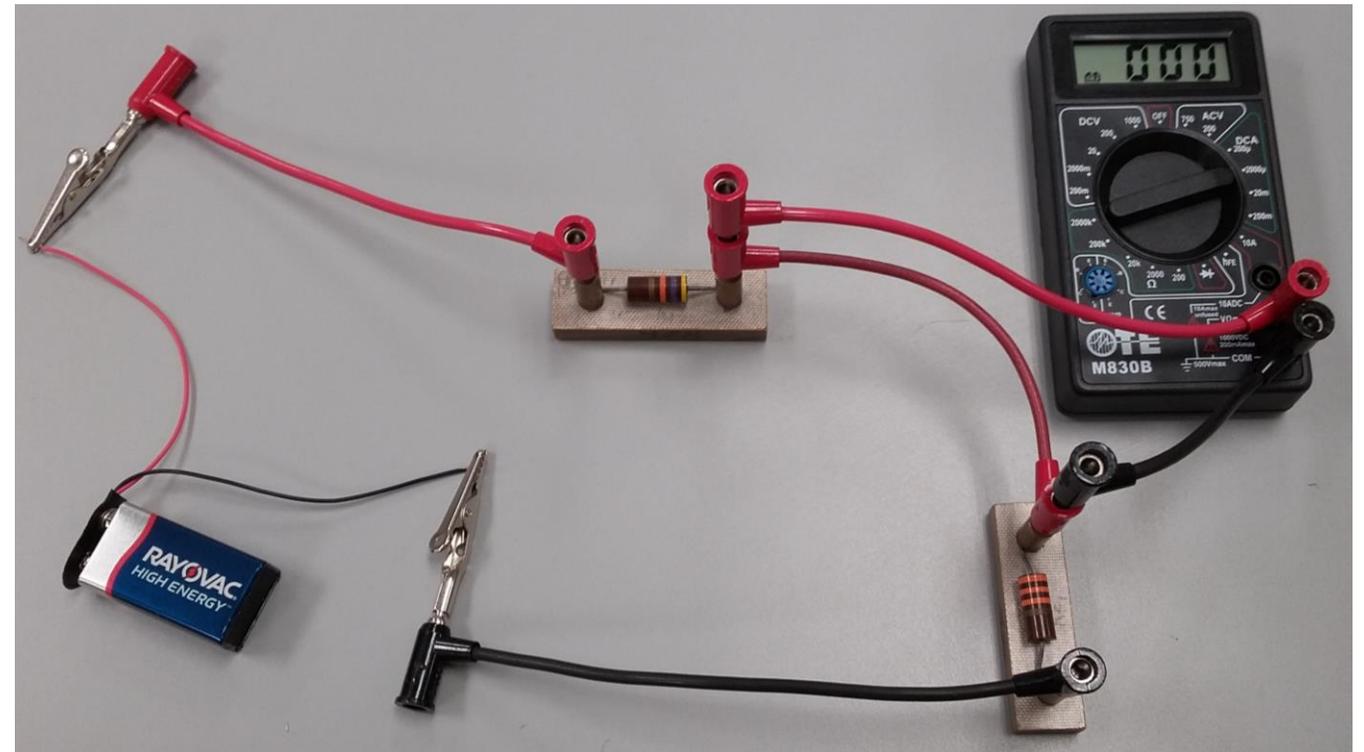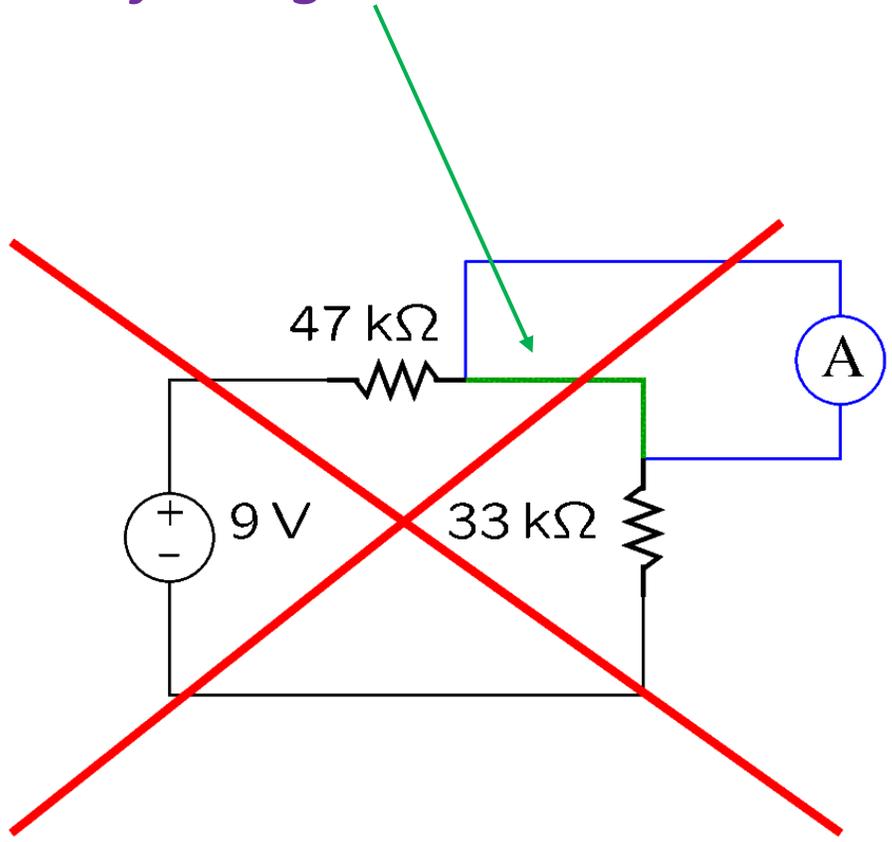
# How to Measure Current—Example (Continued)

- *Current cannot be measured across a wire.*
- *If the green wire is removed, the DMM will display the correct value.*


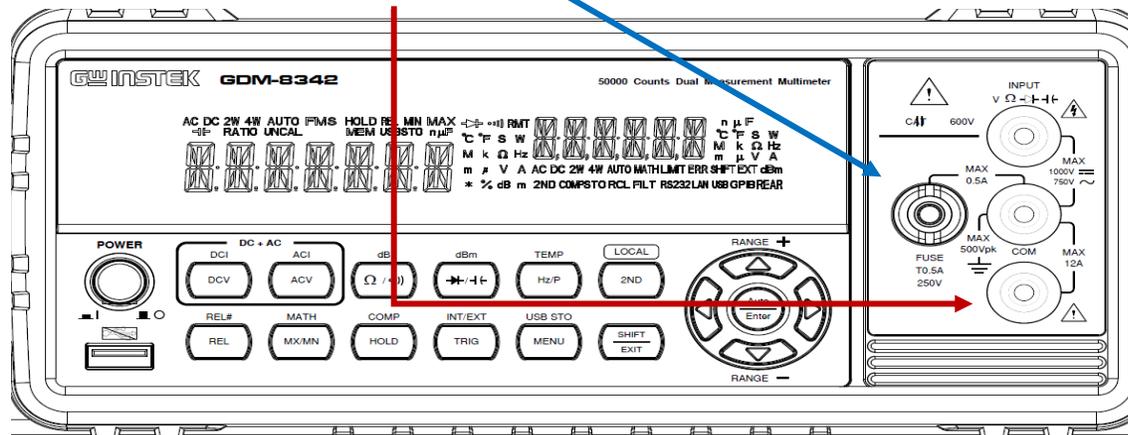
# Ammeters

- DMMs can measure current on several ranges.
- Typical ranges are **200  $\mu$ A**, **2 mA**, **20 mA**, **200 mA**, **2 A**, **20 A**.
- You can select the range that the DMM should use.
- The range value indicates the maximum current that can be measured on that range.
- There are two current terminals:
  - The **terminal** for the **low-current ranges** (below 1A).
  - The **terminal** for the **high-current ranges** (1A and above).



# Ammeters

- In a **range below 1 A**, the DMM measures the current of the terminal for **low-current ranges**.
- In a **range above 1 A**, the DMM measures the current of the terminal for **high-current ranges**.

*Example 1: A 3.7 mA current flowing into the **low-current terminal** should be measured.*

- *In the 200  $\mu\text{A}$  range, the DMM will display OL (**overload**, since  $3.7 \text{ mA} > 200 \mu\text{A}$ .)*
- *In the 2 mA range, the DMM will display OL (**overload**, since  $3.7 \text{ mA} > 2 \text{ mA}$ .)*
- *In the 20 mA and 200 mA ranges, the DMM will display **3.7 mA**.*
- *In the 2 A and 20 A ranges, the value displayed by the DMM will be **incorrect**, since the high current ranges measure the other terminal (the high current terminal).*

# Ammeters

*Example 2: A 75 mA current flowing into the **high current terminal** should be measured.*

- In the 200  $\mu\text{A}$ , 2 mA, 20 mA and 200 mA ranges, the value displayed by the DMM will be **incorrect**, since the low current ranges measure the other terminal.*
- In the 2 A and 20 A ranges, the DMM will display **0.075 A** (which is correct.)*
- Using a terminal for low-current ranges when measuring a high current will result in a reading of zero, because the fuse will be blown.
- When measuring an unknown current, assume a large current value and use the high current terminal (so as to protect the instrument).
- If the current turns out to be low, use the low current terminal for better accuracy.

# DC Power Sources

# Batteries

- Are DC sources of voltage.
- Batteries are made of one or more **cells** connected in series and/or parallel.
  - Connected in series, the voltage output equals the sum of the voltages of each cell.
  - Connected in parallel, the voltage output is the same as the voltage of one cell.
- An **electrolyte** is an electrically conducting solution that contains ions.
- An **electrode** is an electrical conductor used to make contact with the electrolyte.
- A cell consists of electrolyte and two electrodes.



*The six 1.5 V series-connected cells of a 9 V battery.*

# Batteries

- The capacity of a battery is commonly given in **ampere-hours** (A-h).
- In principle, a 3 A-h battery could deliver 1 A for 3 hours.
- In practice, the current is limited by the internal resistance of the battery.
  - A fresh battery has a negligible internal resistance (approximately  $0 \Omega$ .)
  - A discharged battery will have a high internal resistance.
- A fresh battery resembles an ideal **source of voltage**.

# DC Power Supplies


- Consist of electronic circuits that convert the AC supply of the wall outlet to DC.
- Typically, they can operate in
  - constant voltage (CV) mode.
  - constant current (CC) mode.
- The internal resistance of DC power supplies is negligible.
  - In CV mode, the source resembles an ideal [source of voltage](#).
  - In CC mode, the source resembles an ideal [source of current](#).



*A triple DC power supply.*
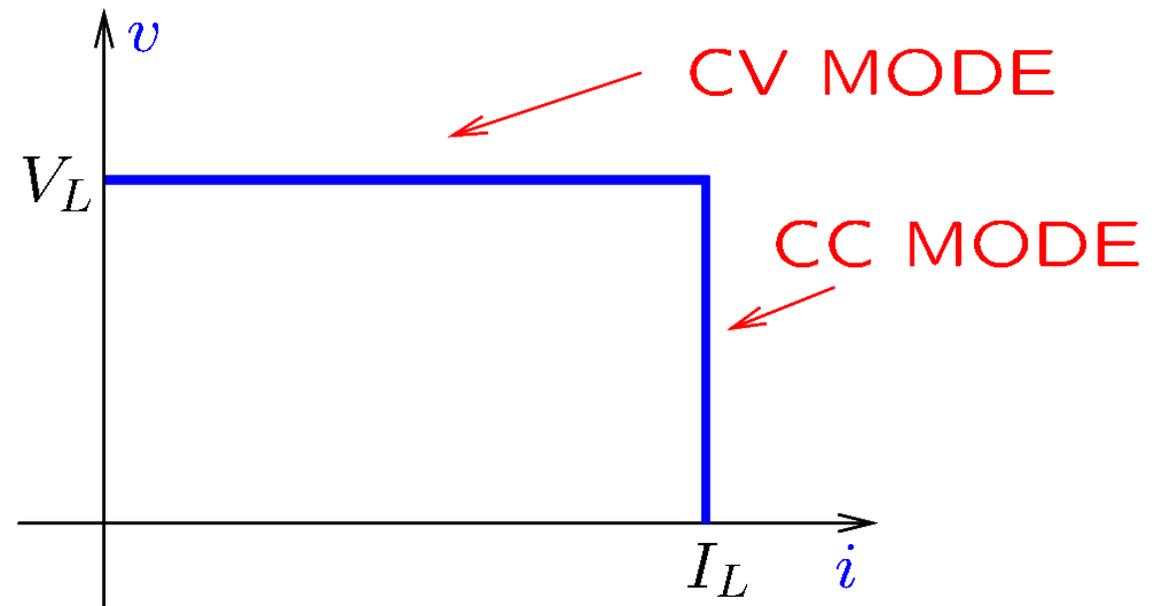
# DC Power Supplies



- When using the power supply:
  - Set the **voltage limit**  $V_L$ . This will be the voltage in CV mode.
  - Set the **current limit**  $I_L$ . This will be the current in CC mode.
- Let  $v$  be the output voltage and  $i$  the output current.
- If the source powers a circuit requiring a current  $i < I_L$  at the voltage  $V_L$ , then the source operates in CV mode at  $v = V_L$ .
- If the circuit requires a voltage  $v < V_L$  at the current  $i = I_L$ , then the source operates in CC mode at  $i = I_L$ .
- At any time, either  $v = V_L$  or  $i = I_L$ .


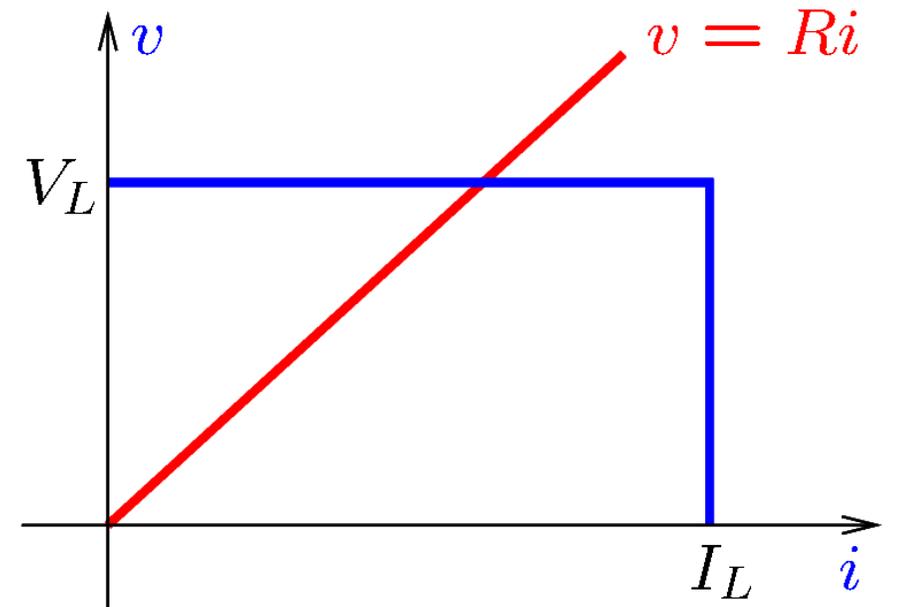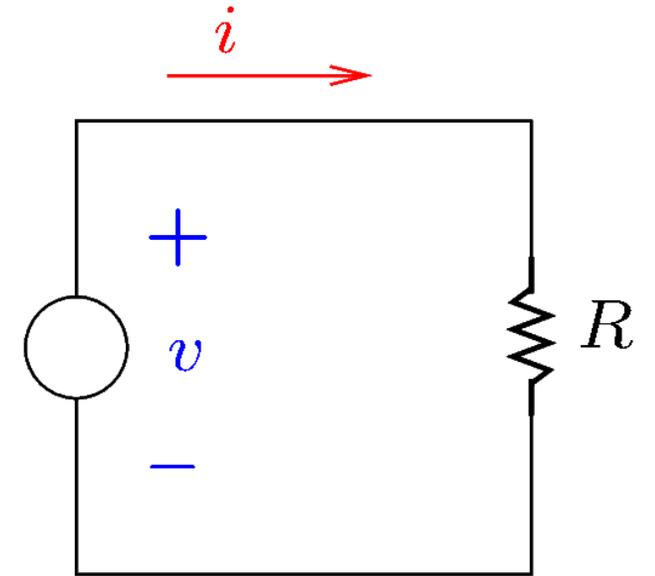
# DC Power Supplies—Example

Assuming a CV/CC supply with  $V_L = 12\text{ V}$  and  $I_L = 2\text{ A}$ , find the voltage and current for a load of resistance  $R = 10\ \Omega$ .

- By Ohm's law,  $v = Ri$ .
- When  $v = 12\text{ V}$ ,  $i = \frac{v}{R} = 1.2\text{ A}$ .
- The curve  $v = Ri$  is shown in red.
- The intersection point of the blue and red curves gives the operating point:  
 $v = 12\text{ V}$  and  $i = 1.2\text{ A}$ .
- Note that the source operates in CV mode.



# DC Power Supplies—Example

Assuming a CV/CC supply with  $V_L = 12\text{ V}$  and  $I_L = 2\text{ A}$ , find the voltage and current for a load of resistance  $R = 4\ \Omega$ .

- By Ohm's law,  $v = Ri$ .
- When  $v = 12\text{ V}$ ,  $i = \frac{v}{R} = 3\text{ A}$ .
- The curve  $v = Ri$  is shown in red.
- The intersection point of the blue and red curves gives the operating point:  
 $i = 2\text{ A}$  and  $v = Ri = 8\text{ V}$ .
- Note that the source operates in CC mode.

