

Sources, Multimeters, and Transformers

M.V. Iordache, *EEGR2051 Circuits and Measurements Lab*, Fall 2020, LeTourneau University
See <https://mviordache.name/EEGR2051> for more information.

DC Power Supplies

DC Power Supplies—Review


- Consist of electronic circuits that convert the AC supply of the wall outlet to DC.
- Typically, they can operate in
 - constant voltage (CV) mode.
 - constant current (CC) mode.
- The internal resistance of DC power supplies is negligible.
 - In CV mode, the source resembles an ideal **source of voltage**.
 - In CC mode, the source resembles an ideal **source of current**.



A triple DC power supply.

DC Power Supplies—Review

- When using the power supply:
 - Set the **voltage limit** V_L . *This will be the voltage in CV mode.*
 - Set the **current limit** I_L . *This will be the current in CC mode.*
- Let v be the output voltage and i the output current.
- If the source powers a circuit requiring a current $i < I_L$ at the voltage V_L , then the source operates in CV mode at $v = V_L$.
- If the circuit requires a voltage $v < V_L$ at the current $i = I_L$, then the source operates in CC mode at $i = I_L$.
- At any time, either $v = V_L$ or $i = I_L$.

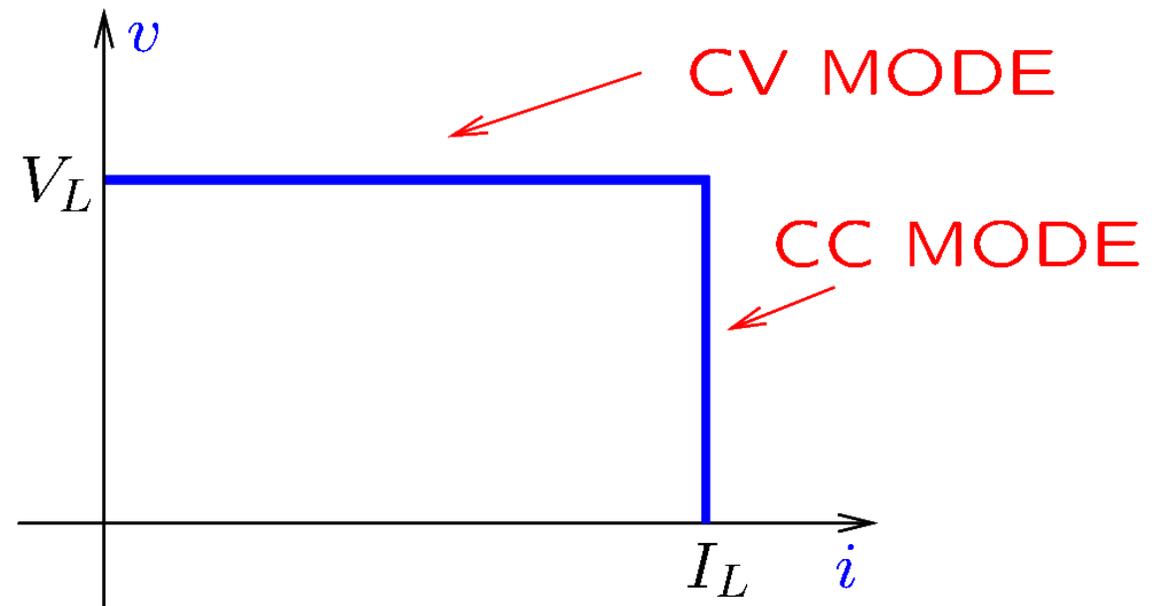


DC Power Supplies

Example: A DC power supply has $V_L = 10\text{ V}$ and $I_L = 4\text{ A}$. Find the short-circuit current.

- Ideally, the resistance of a short-circuit is zero.
- Therefore, $v = 0$.
- The curve indicates that $i = I_L$ when $v = 0$. The answer is $i = 4\text{ A}$.

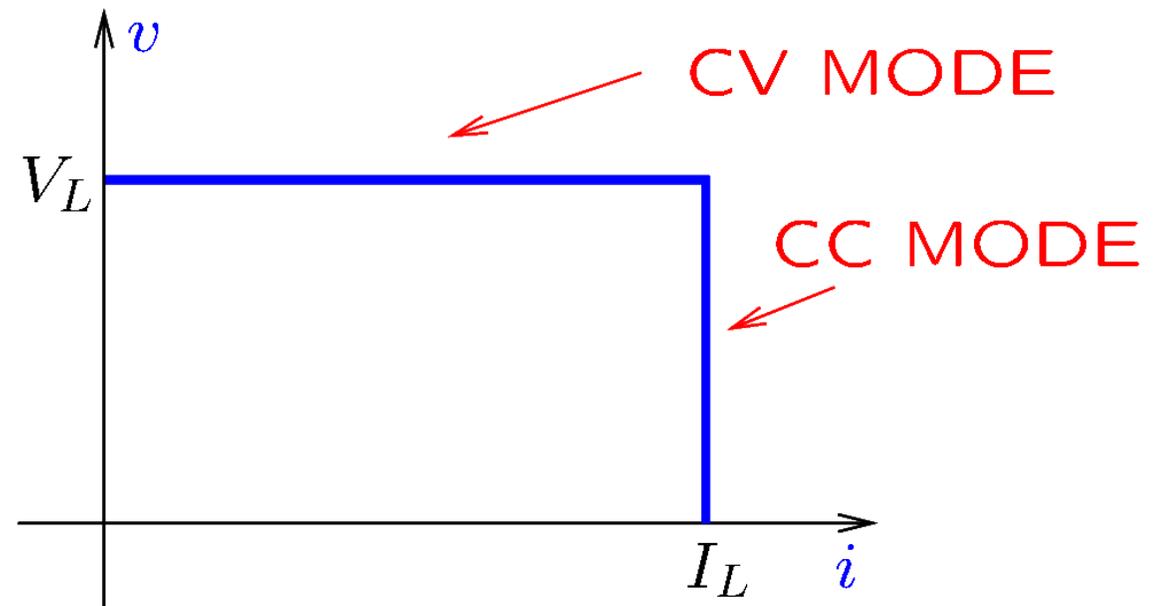Example: In the previous example, what is the open-circuit voltage?

- An open circuit implies $i = 0$.
- The curve indicates that $v = V_L$ when $i = 0$. The answer is $v = 10\text{ V}$.





DC Power Supplies

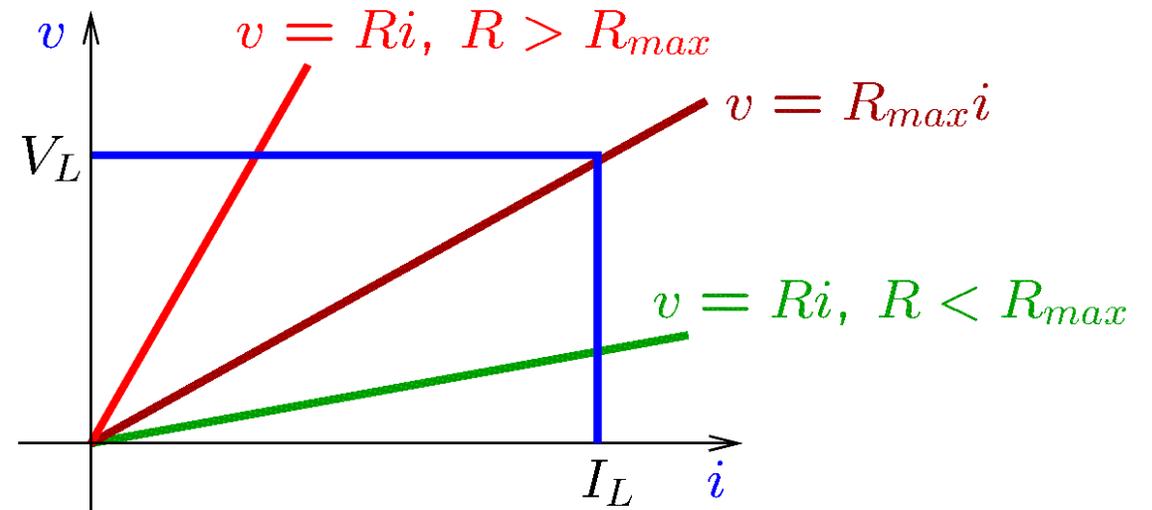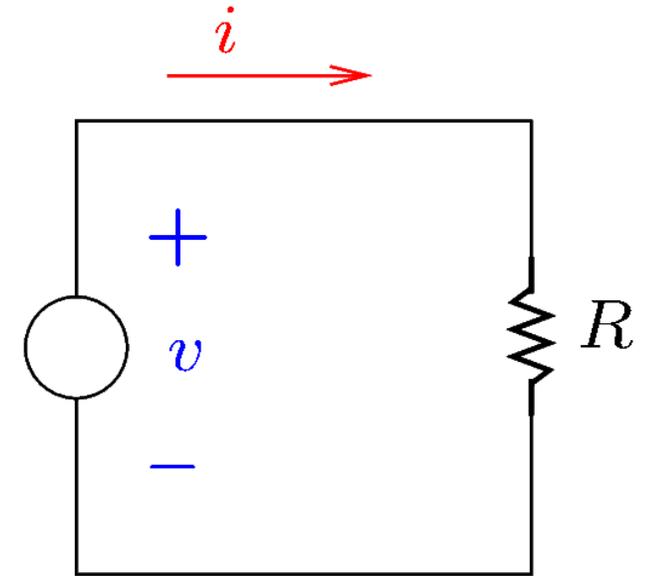Example: Assuming a CV/CC supply with $V_L = 15\text{ V}$ and $I_L = 3\text{ A}$, find the maximum value of R for which the load operates in CC mode.


- By Ohm's law, $v = Ri$.
- The equation $v = Ri$ describes a line of slope R .
- The maximum slope for which the line intersects the curve of the source in the CC region is

$$R_{max} = \frac{V_L}{I_L} = 5\ \Omega$$





Adjusting Current and Voltage

- If the voltage of a DC source cannot be changed, a simple way to adjust the load current is with a *rheostat*.
- A rheostat is a variable resistor rated for high power levels.
- In a *slide rheostat*:
 - Resistive wire wound around an insulating tube forms a resistor.
 - Let X and Y be the resistor terminals.
 - A *slider*, also known as *wiper*, slides on a conductive bar B while touching the resistive wire.
 - By moving the slider left or right, it is possible to vary the resistance between B and X or B and Y .

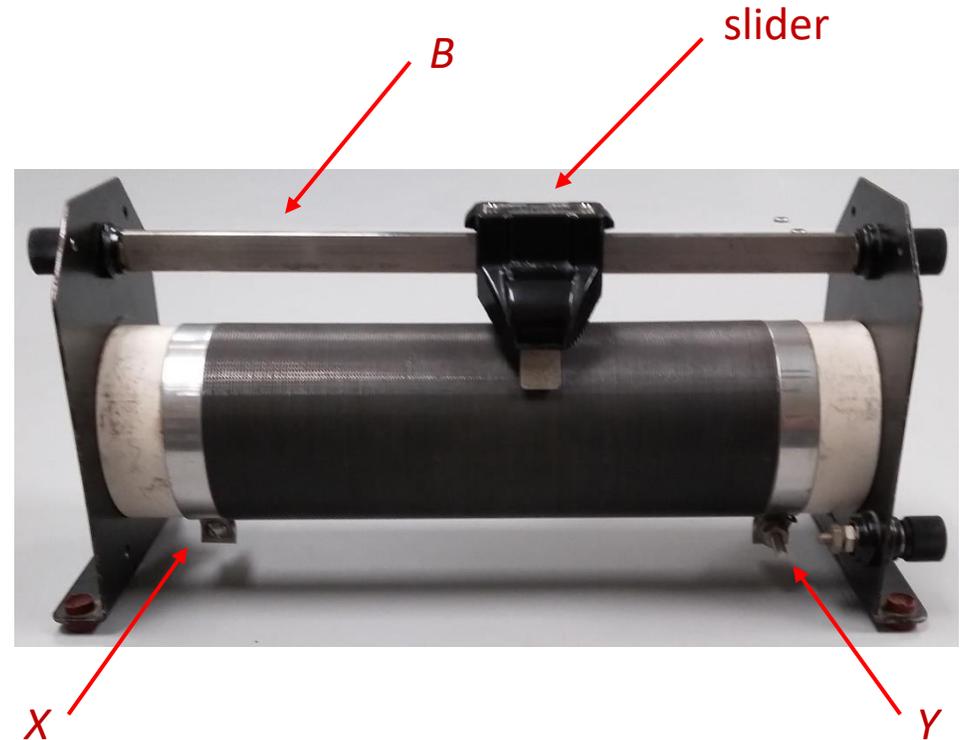


Adjusting Current and Voltage

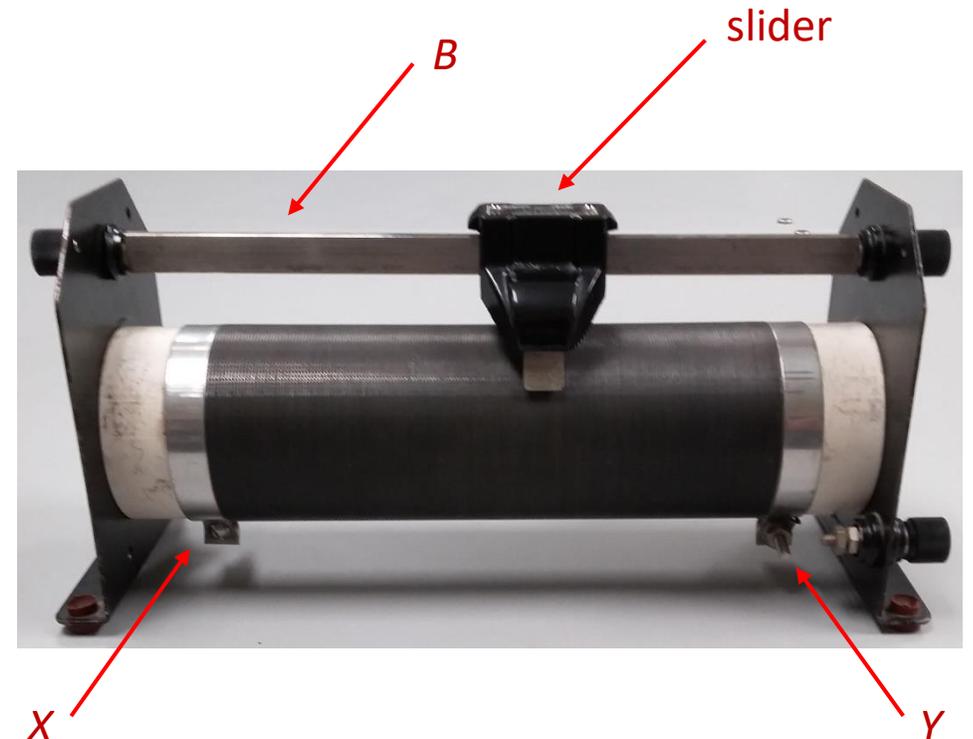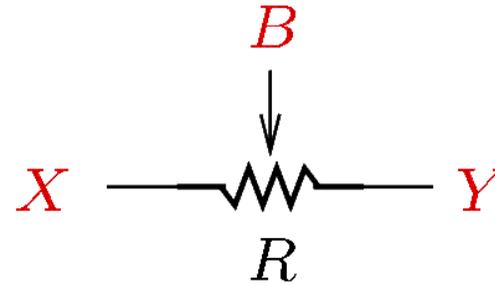- A rheostat may be represented by the symbol of a variable resistor.
- Let R be the resistance of the rheostat, that is, the resistance between the points X and Y .
- As the slider is moved from X to Y :
 - The resistance between X and B is varied from 0 to R .
 - The resistance between Y and B is varied from R to 0 .



Adjusting Current and Voltage

- When a load requires a small amount of current, a simple way to change its voltage is with a *potentiometer*.
- A potentiometer is a variable resistor rated for low power levels.
- A potentiometer has:
 - A resistive track connected to the left and right terminals.
 - A wiper connected to the middle terminal and attached to a rotating shaft.
- The wiper touches the resistive track.
- By turning the shaft, the resistance between the middle terminal and the right/left terminals is varied.

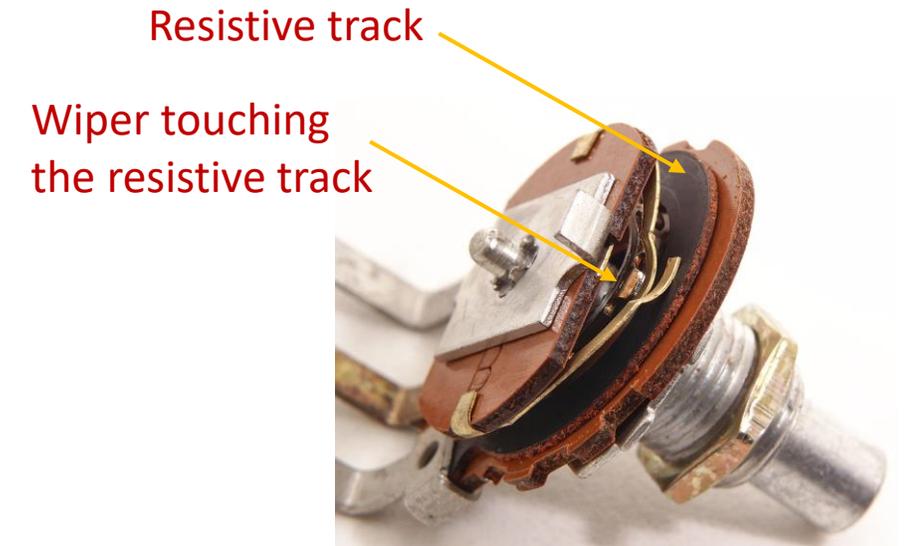

Images from <https://commons.wikimedia.org/wiki/File:Electronic-Component-Potentiometer.jpg>
and https://commons.wikimedia.org/wiki/File:Single-turn_potentiometer_with_internals_exposed_oblique_view.jpg

Adjusting Current and Voltage—Example

A 12 V source is connected in series with a 2 Ω load and a 22 Ω rheostat.


- When the rheostat is adjusted to 0 Ω, the load current is $I = \frac{12\text{ V}}{2\ \Omega} = 6\text{ A}$.
- To reduce the current to $I = 1.5\text{ A}$, the rheostat has to be adjusted to a value r satisfying

$$\frac{12\text{ V}}{r + 2\ \Omega} = 1.5\text{ A} \Rightarrow r = 6\ \Omega$$

- The load voltage is $V_L = 2\ \Omega \cdot 1.5\text{ A} = 3\text{ V}$.
- At $I = 1.5\text{ A}$, the efficiency of the system is

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_L \cdot 1.5\text{ A}}{12\text{ V} \cdot 1.5\text{ A}} = 25\%$$

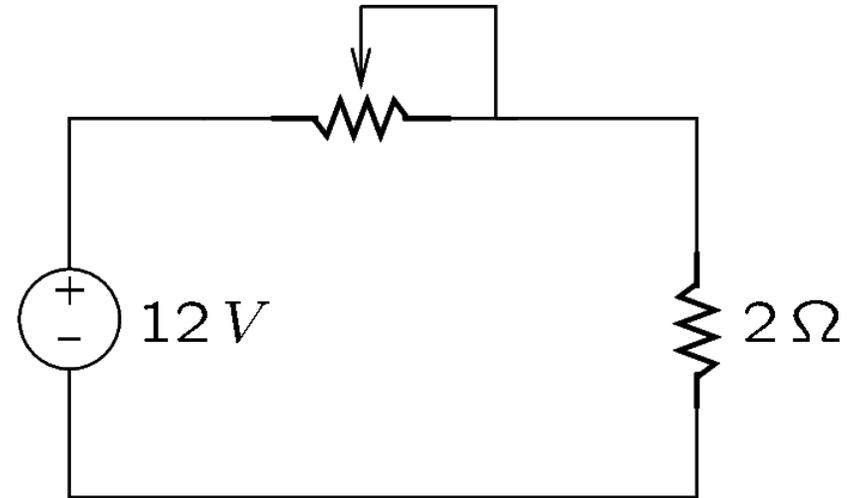- *A rheostat provides a simple but inefficient way of controlling current.*



Multimeters

Measurement Range

- DMMs perform measurements within a prespecified *range*.
 - For example, typical current ranges are $200\ \mu\text{A}$, $2\ \text{mA}$, $20\ \text{mA}$, $200\ \text{mA}$, $2\ \text{A}$, $20\ \text{A}$.
- The range indicates the maximum value that can be measured.
 - For example, if the range is set to $20\ \text{mA}$ and a $30\ \text{mA}$ current is to be measured, then the DMM will indicate **OVERLOAD**.
 - To measure the $30\ \text{mA}$ current, the range must be changed to $200\ \text{mA}$.
- A range can be changed by pressing the arrow keys.
 - When an arrow key is pressed, the DMM enters the **MANUAL** mode.
- If the **AUTO** key is pressed, the DMM selects automatically the right range.



Current Measurements

- DMMs typically have two current terminals:
 - The **terminal** for **low-current ranges** (typically, below 1A).
 - The **terminal** for **high-current ranges** (typically, above 1A).



Current Measurements

How to know which terminal the DMM uses when performing a current measurement?

- A DMM in **AUTO** mode will measure the current of the **low-range** terminal.
- A DMM in **MANUAL** mode will measure the current of the **low-range** terminal when **the range is less than 1 A**.
- A DMM in **MANUAL** mode will measure the current of the **high-range** terminal when **the range is over 1 A**.
- *DMMs use the high-range terminal only when in MANUAL mode on a range above 1 A.*

Current Measurements—Examples

A DMM has the following current ranges: $200\ \mu\text{A}$, $2\ \text{mA}$, $20\ \text{mA}$, $200\ \text{mA}$, $2\ \text{A}$, $20\ \text{A}$. A current in the range $50 \dots 150\ \text{mA}$ should be measured.

- *Solution 1:* Use the *low-range* terminal and AUTO mode.
- *Solution 2:* Use the *low-range* terminal, MANUAL mode, and the $200\ \text{mA}$ range.
- *Solution 3:* Use the *high-range* terminal, MANUAL mode, and the $2\ \text{A}$ range.

Assume now that the unknown current is in the range $300 \dots 600\ \text{mA}$.

- *Solution:* Use the *high-range* terminal, MANUAL mode, and the $2\ \text{A}$ range.


The Loading Effect

- Ideally, an instrument will not change the value of the variable it measures.
- However, DMMs connected to a circuit act as additional circuit loads and change somewhat the currents and voltages they measure.
- This is known as *the loading effect*.
- In most cases, when a DMM is used correctly, the loading effect is not significant.
- To avoid measurement error, it is necessary to determine whether a DMM loads considerably a circuit.

The Loading Effect—Voltage Measurements

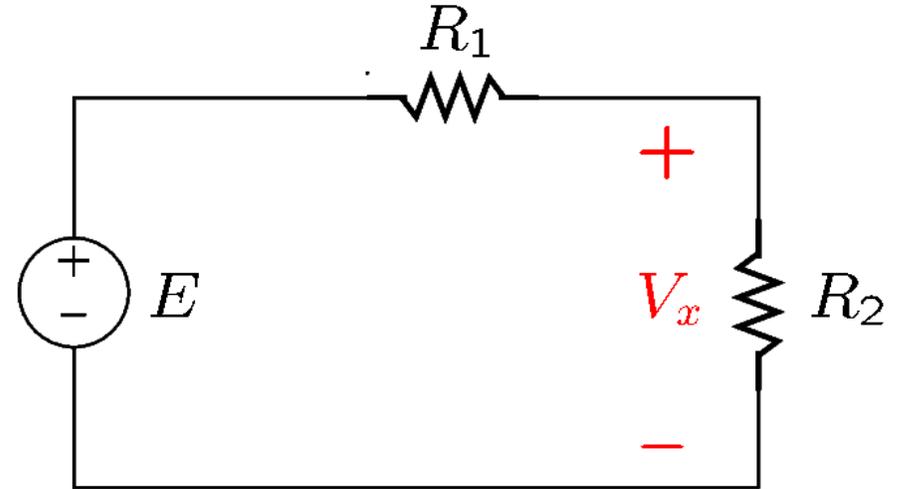
Example: Suppose that the voltage V_x should be measured.

- *A voltmeter is electrically equivalent to a resistor of very large value (such as $10\text{ M}\Omega$).*
- *Let R_v be the internal resistance of the voltmeter.*
- *Adding a voltmeter to the circuit is equivalent to adding a resistor R_v to the circuit.*



The Loading Effect—Voltage Measurements

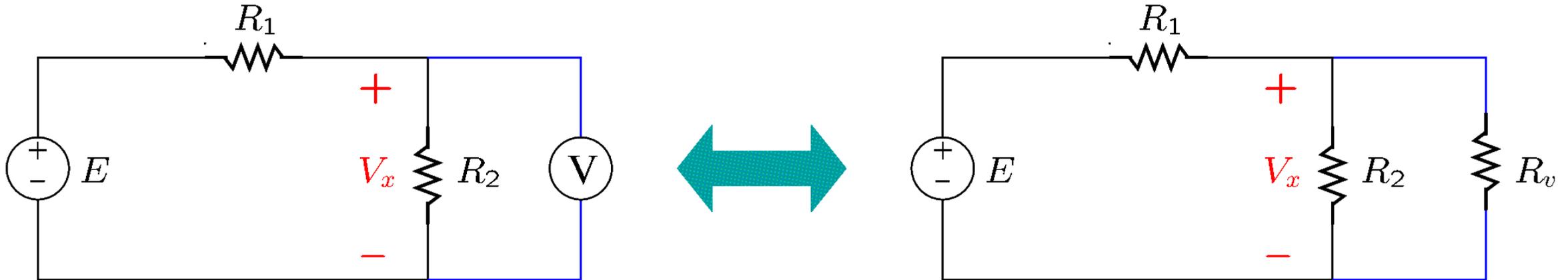
- *Adding a voltmeter to the circuit is equivalent to adding a resistor R_v to the circuit.*



The Loading Effect—Voltage Measurements


- Before connecting the voltmeter,

$$V_x = E \cdot \frac{R_2}{R_1 + R_2}.$$

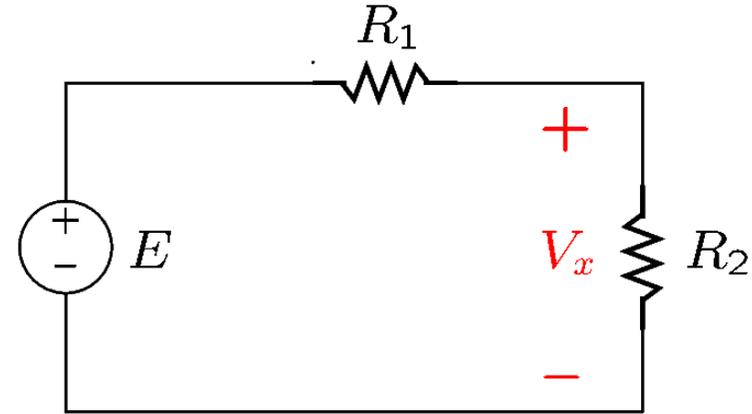

- After connecting the voltmeter,
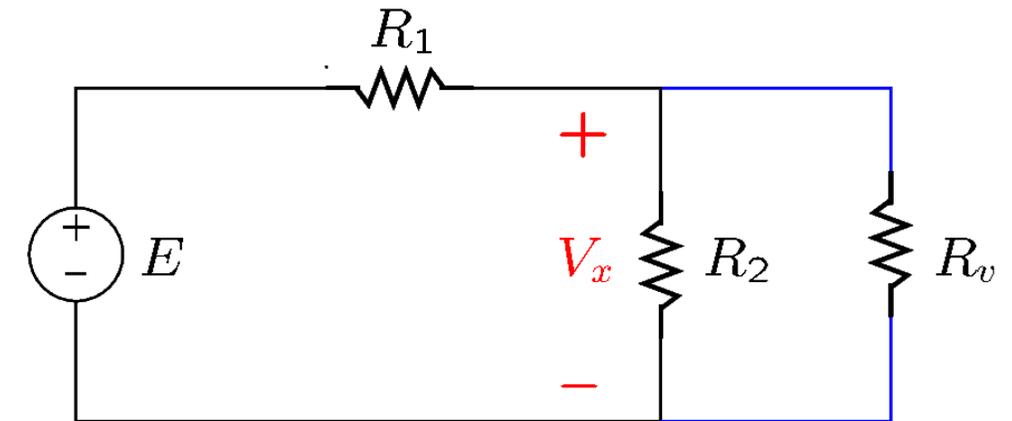
$$V_x = E \cdot \frac{R_2 \parallel R_v}{R_1 + R_2 \parallel R_v}.$$





- The change in voltage is negligible only if R_v is much larger than R_2 .

The Loading Effect—Voltage Measurements

For example, assume $E = 20\text{ V}$, $R_v = 10\text{ M}\Omega$, and $R_1 = R_2$.

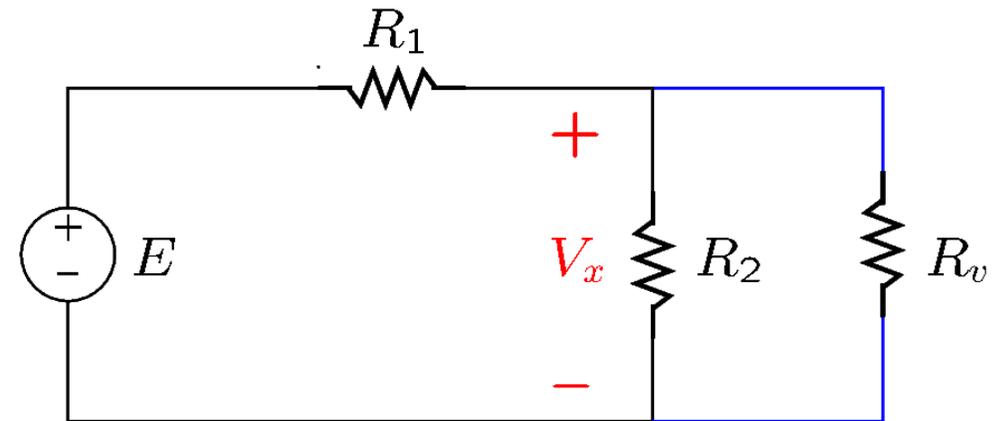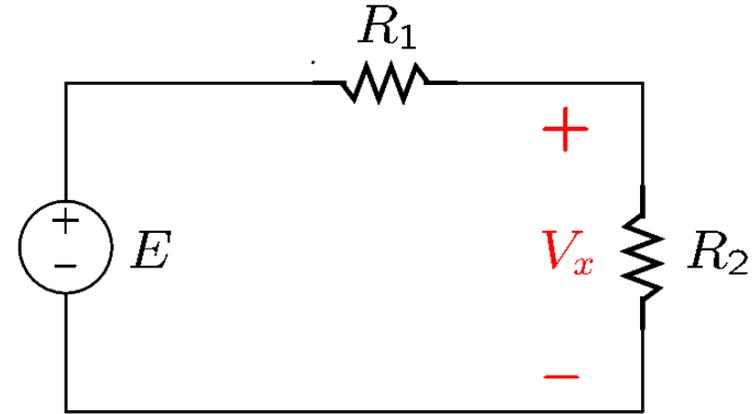
- The actual value of V_x is **10 V**.
- If $R_1 = R_2 = 100\ \Omega$, the measured V_x will be **9.99995 V**.
- If $R_1 = R_2 = 10\text{ k}\Omega$, the measured V_x will be **9.995 V**.
- If $R_1 = R_2 = 1\text{ M}\Omega$, the measured V_x will be **9.524 V**.
- If $R_1 = R_2 = 100\text{ M}\Omega$, the measured V_x will be **1.667 V!**



The Loading Effect—Current Measurements

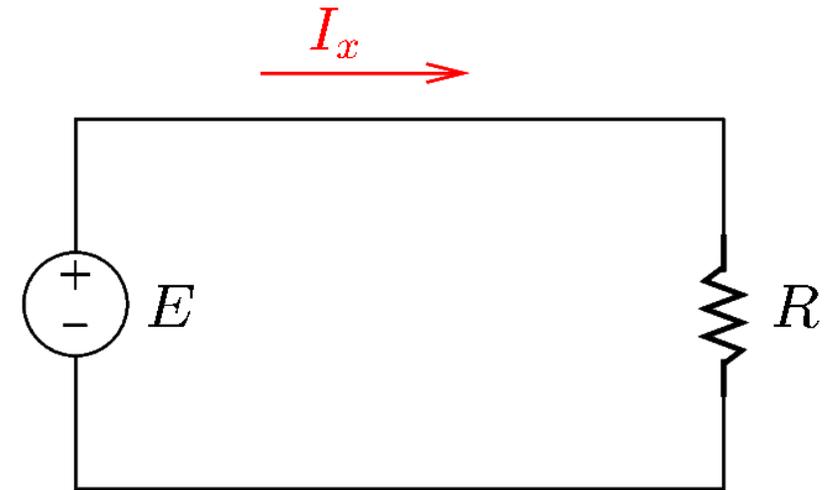
Example: Suppose that the current I_x should be measured.

- An ammeter is electrically equivalent to a resistor of low value (such as $10\ \Omega$).*
- Let R_a be the internal resistance of the ammeter.*
- Adding an ammeter to the circuit is equivalent to adding a resistor R_a to the circuit.*
- Note that R_a is not a constant but depends on range and current terminal (whether the low-range or high-range terminal is used.)*



The Loading Effect—Current Measurements

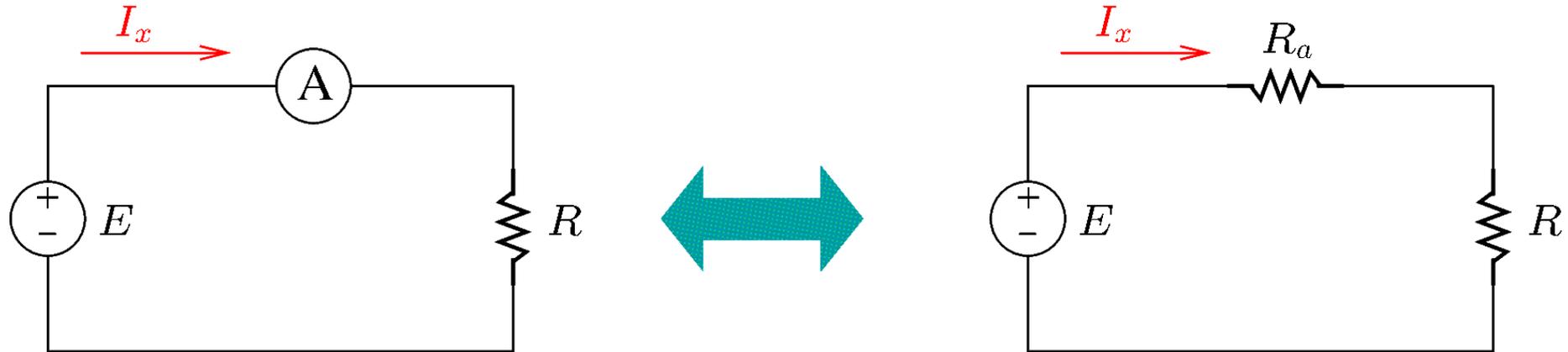
- Adding an ammeter to the circuit is equivalent to adding a resistor R_a to the circuit.



The Loading Effect—Current Measurements


- Before connecting the ammeter,

$$I_x = \frac{E}{R}.$$

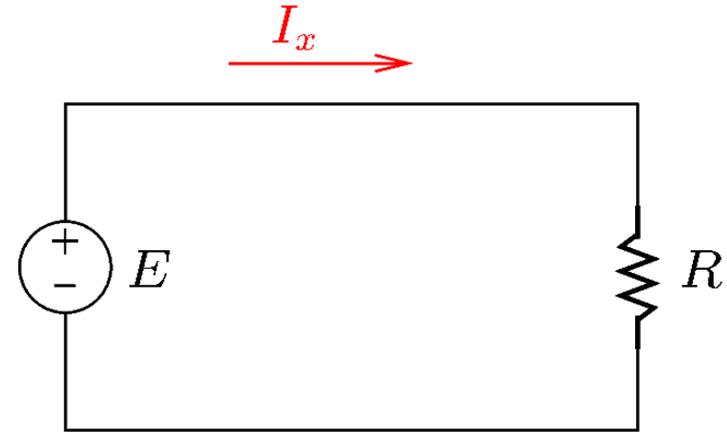

- After connecting the ammeter,

$$I_x = \frac{E}{R+R_a}.$$


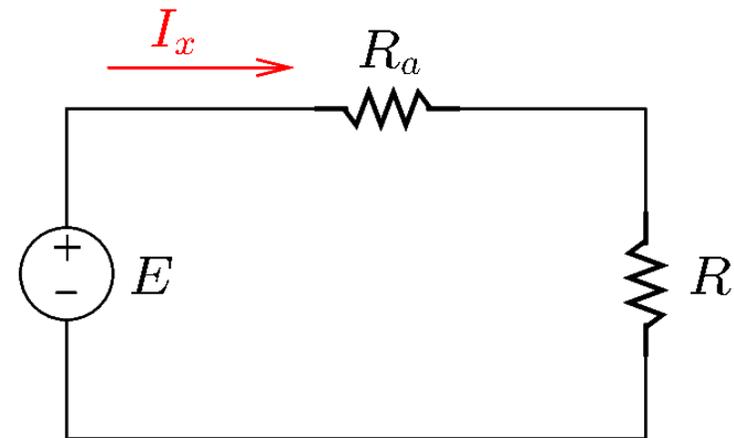


- The change in current is negligible only if R_a is much smaller than R .

The Loading Effect—Current Measurements

For example, assume $E = 20\text{ V}$, $R = 200\ \Omega$, $R_a = 0.1\ \Omega$ on the high range terminal, and $R_a = 1\ \Omega$ on the low range terminal for the 200 mA range.

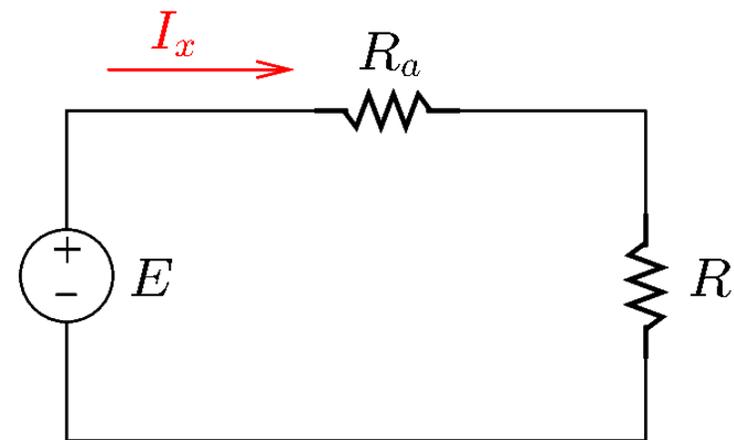
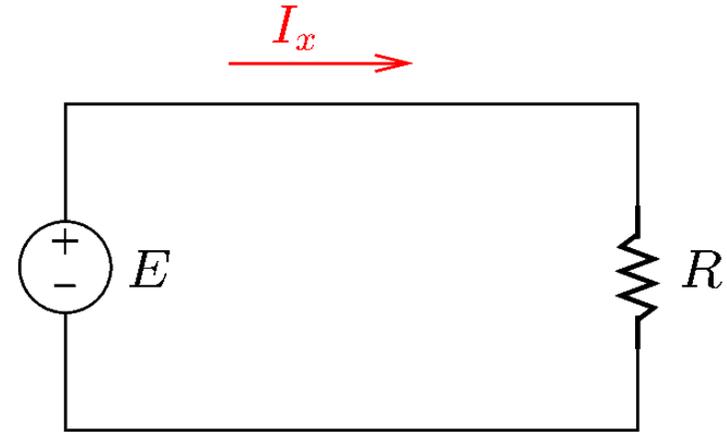
- The actual value of I_x is **100 mA**.
- The value of I_x when measured on the high range terminal is **99.95 mA**.
- The value of I_x when measured on the low range terminal is **99.5 mA**.



Ammeters—Review



- The current of a component is measured by placing the ammeter in series with the component.

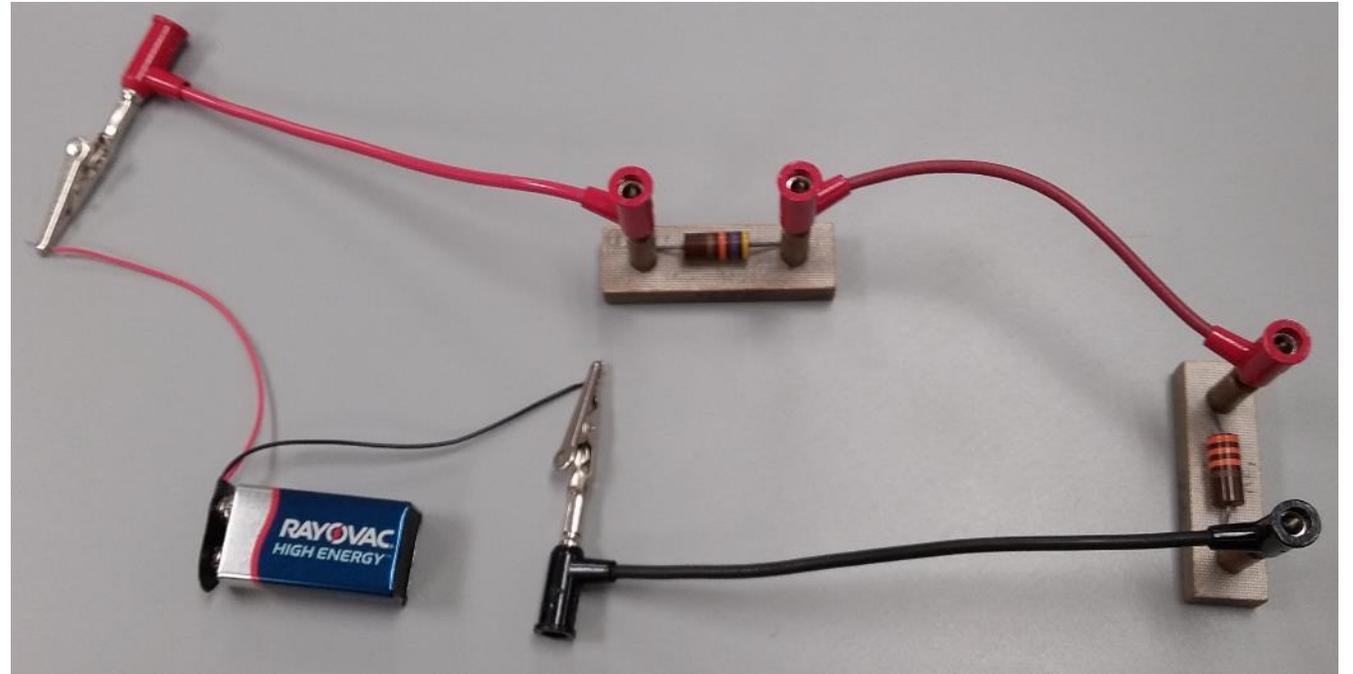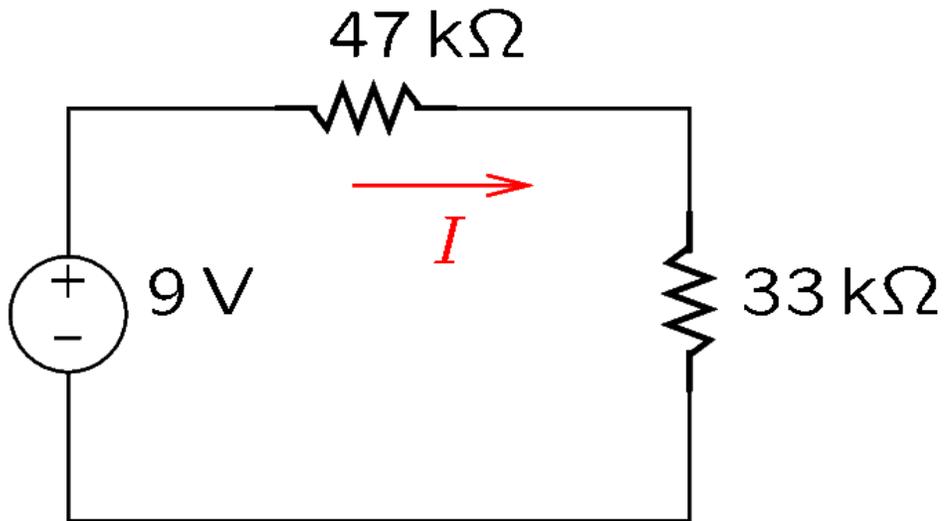Example: The current of the 47 k Ω resistor should be measured.



How to Measure Current—Example (Continued)

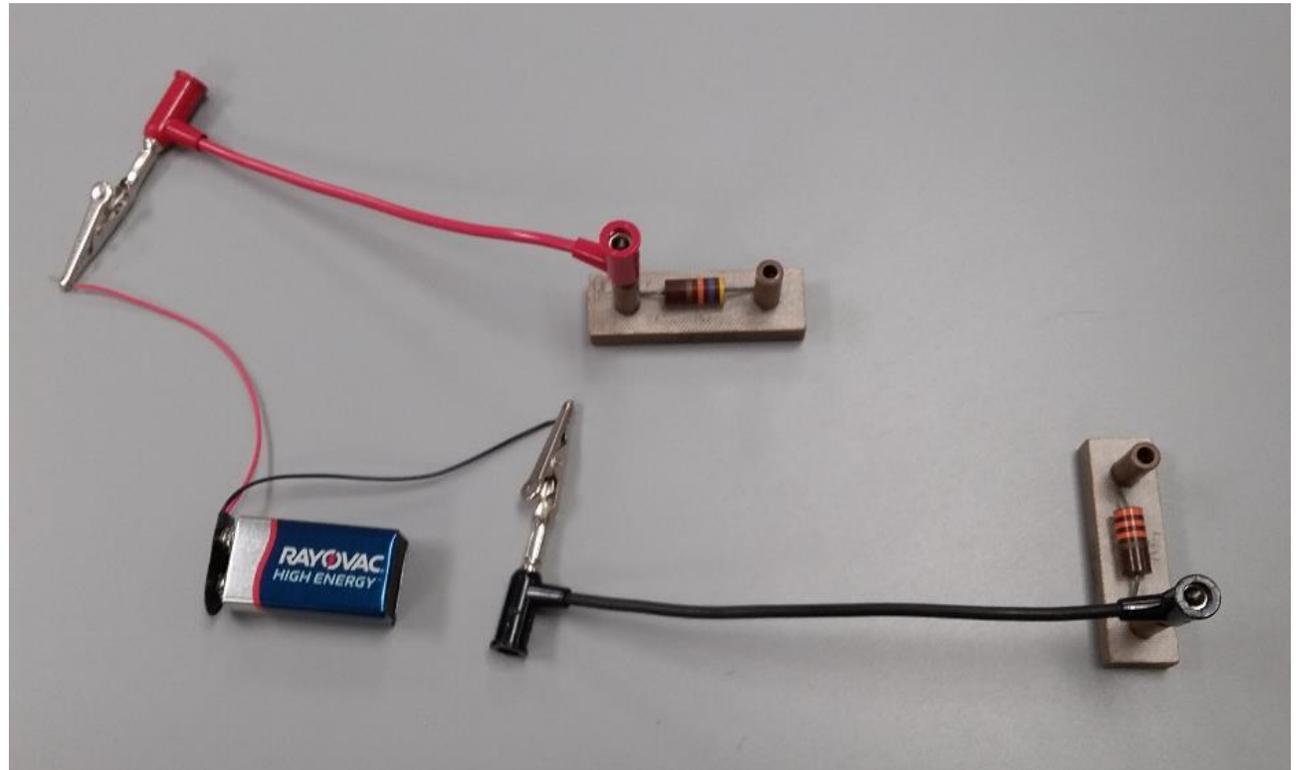
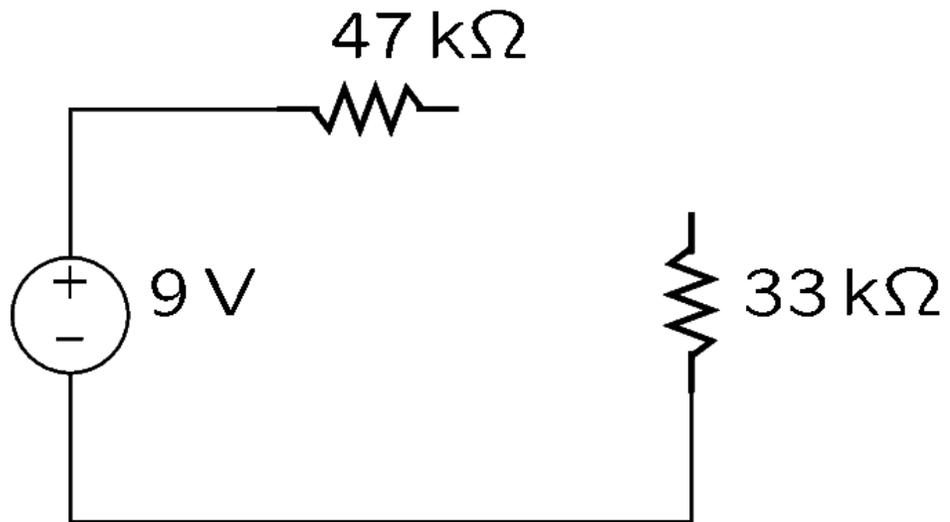
Step 1: Disconnect the resistor at one of its ends.



How to Measure Current—Example (Continued)



Step 2: Reconnect the resistor by means of an ammeter, so that the current to or from the resistor flows through the ammeter.

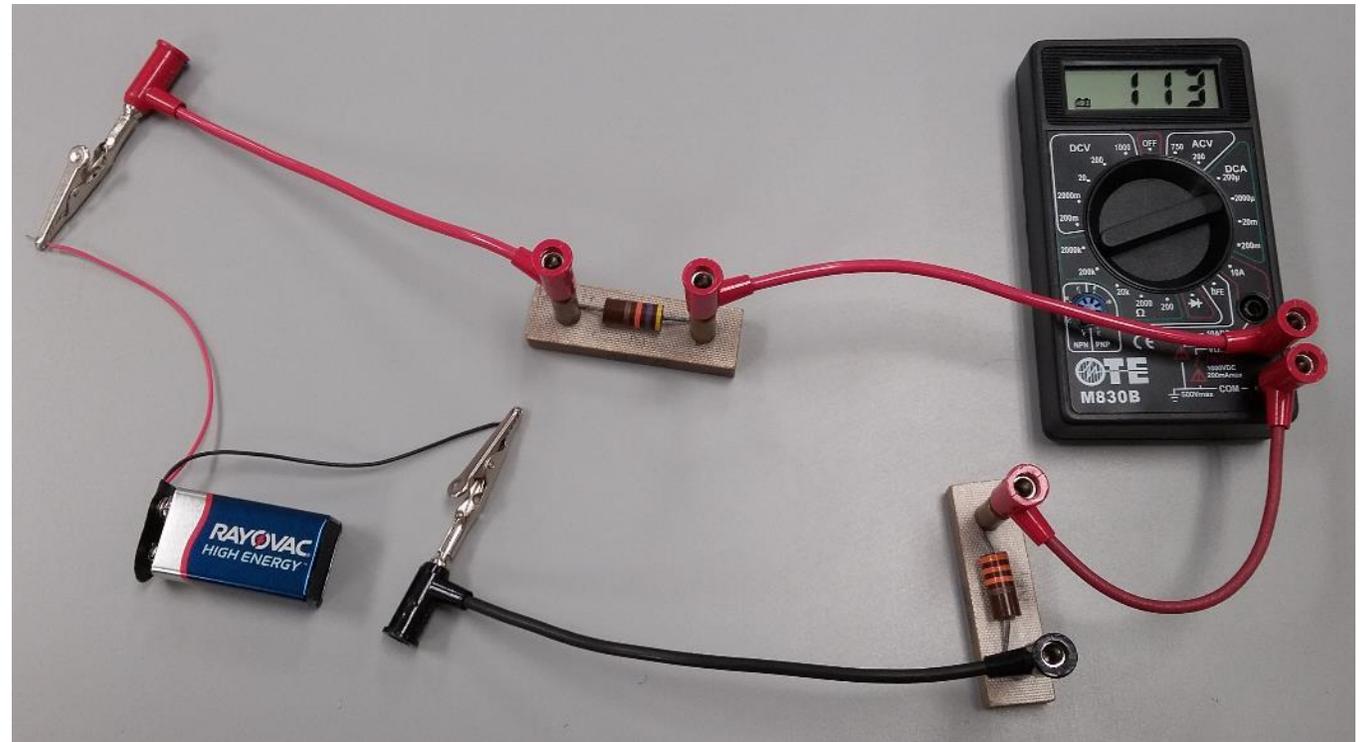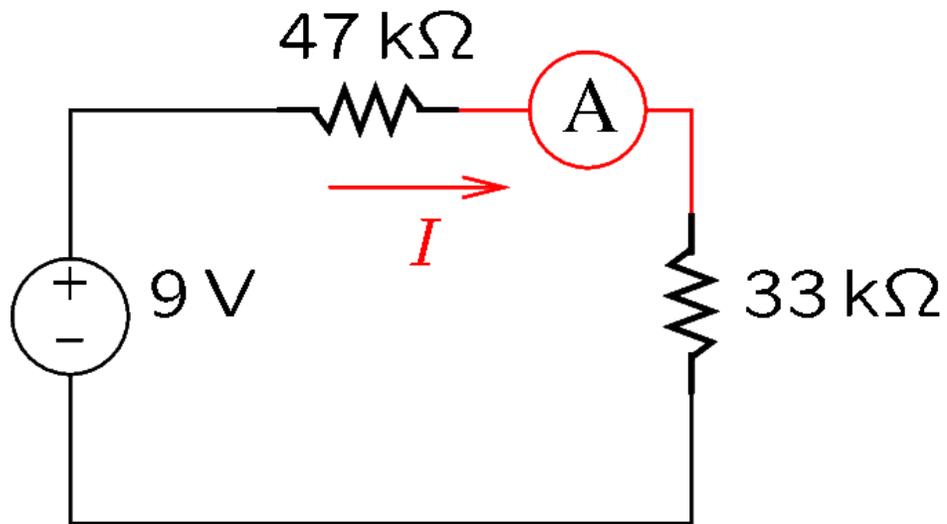The ammeter shows a current $I = 113 \mu\text{A}$.




How to Measure Current—Example (Continued)

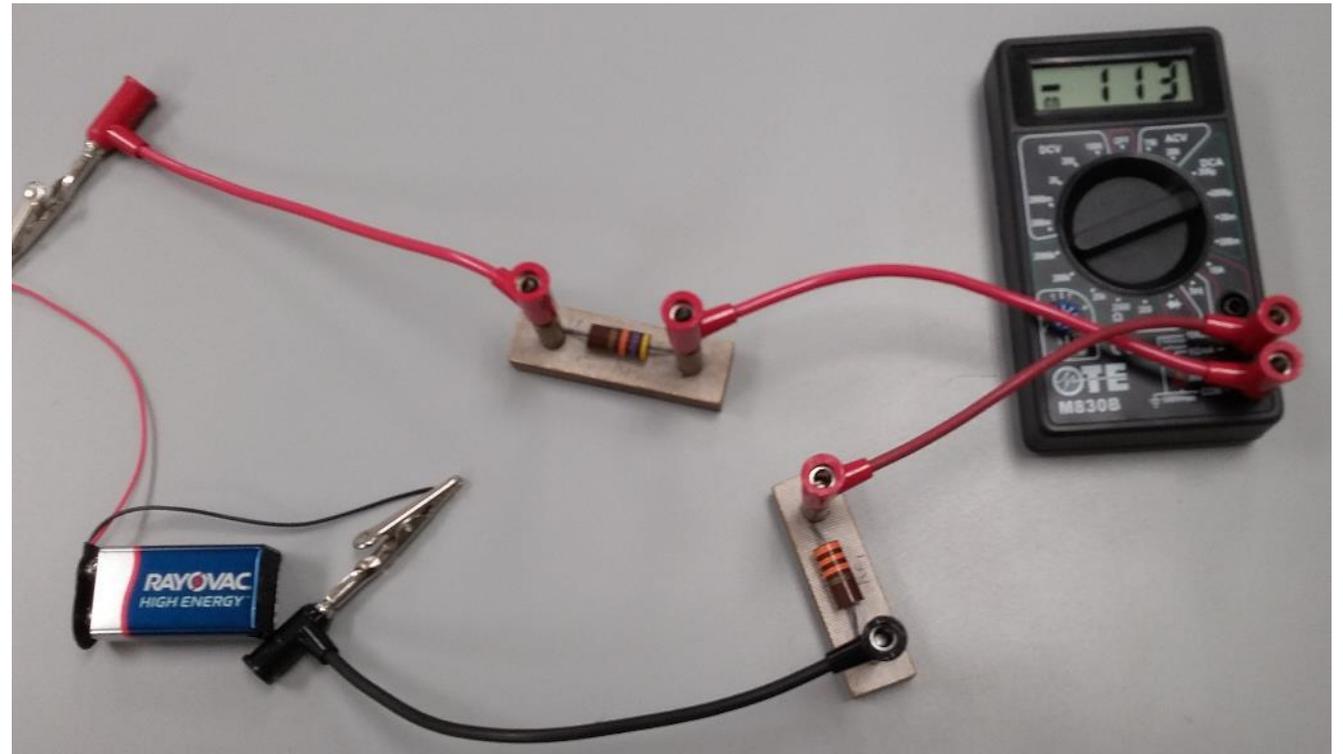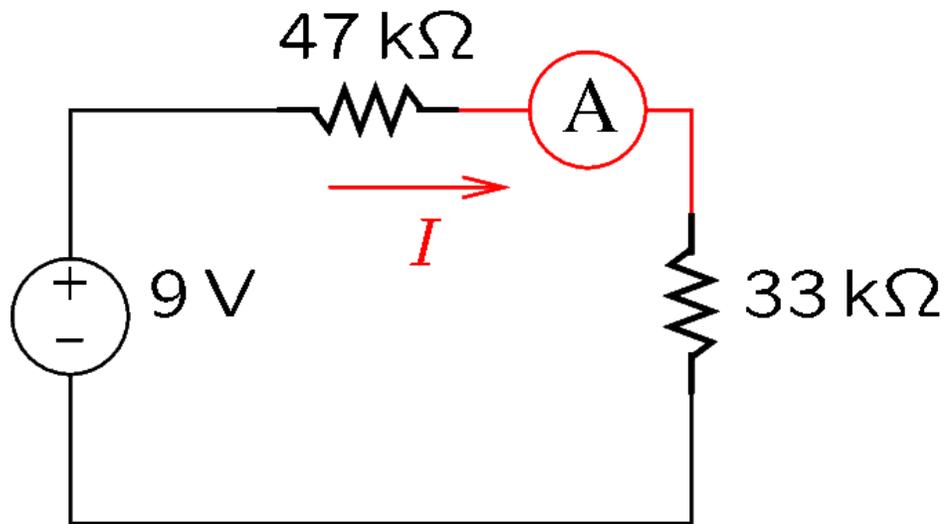Note that by interchanging the connections of the ammeter, the sign of the measured current changes: $-113 \mu\text{A}$ instead of $+113 \mu\text{A}$.




How to Measure Current—Review

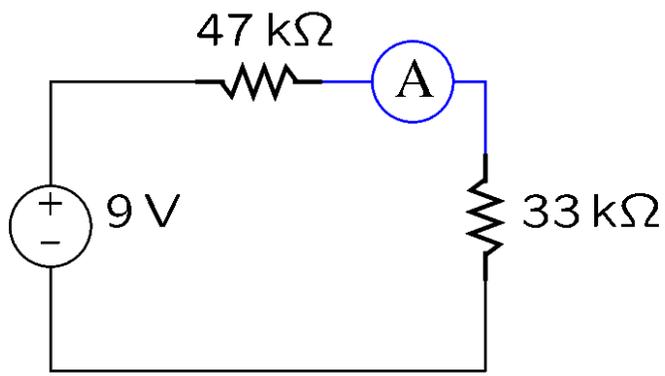- *Ammeters are always connected in series.*
- *An ammeter may not be connected across a component.*
- *Otherwise, the ammeter will show an incorrect value and the ammeter fuse may get blown.*
- *Note that when the fuse is blown, the ammeter indicates a zero current (since no current can flow through it).*





CORRECT

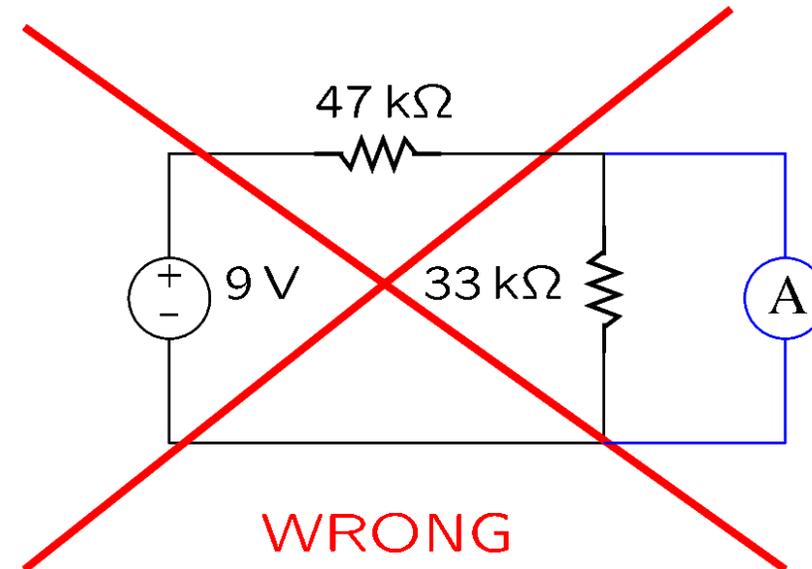

WRONG



How to Measure Current—Example (Continued)

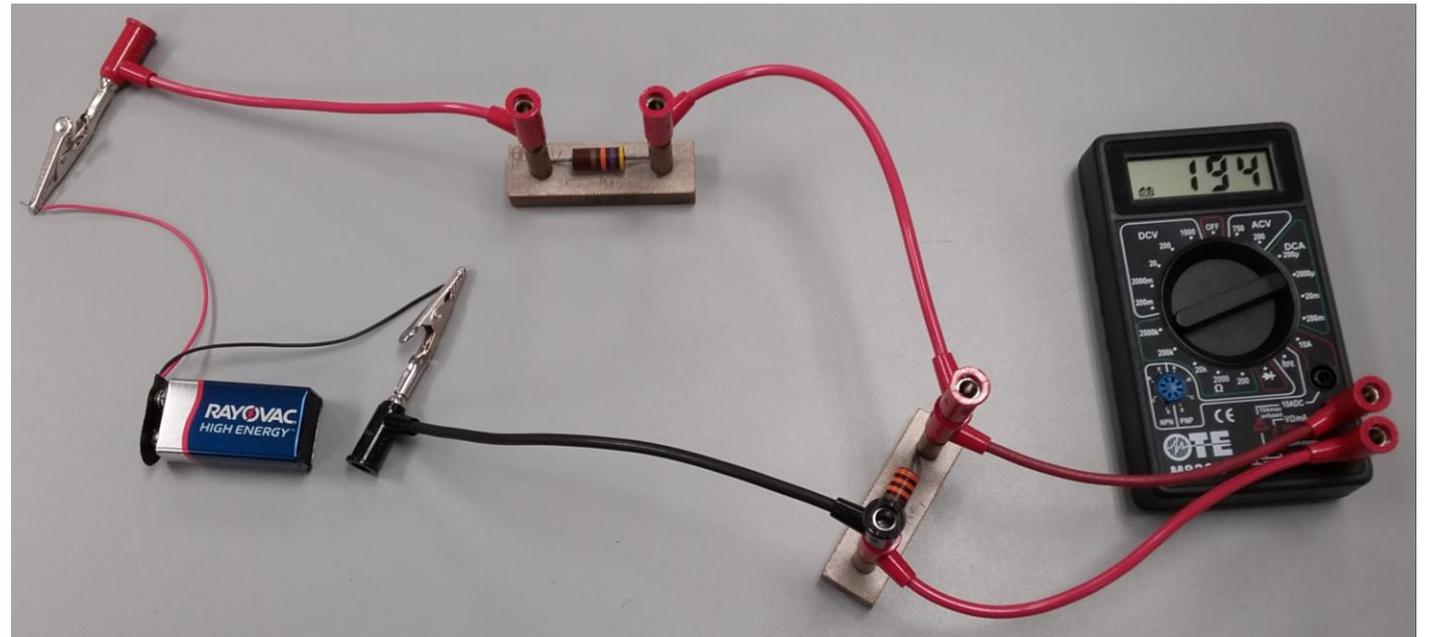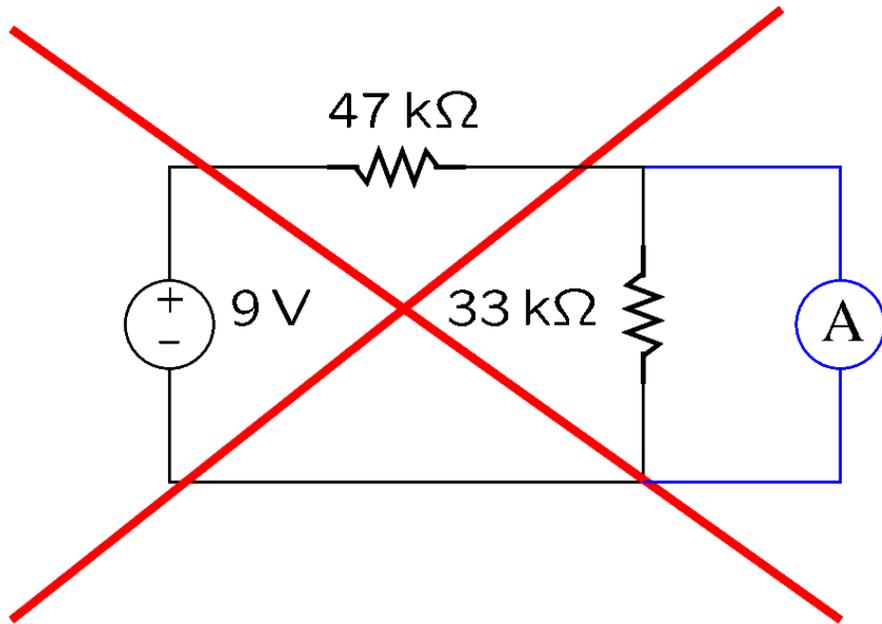- *In the previous example, the current of the $33\text{ k}\Omega$ resistor was $113\ \mu\text{A}$.*
- *The figure below shows an incorrect way to measure this current.*
- *The measurement is wrong because the ammeter is in parallel, not in series.*



How to Measure Current—Example (Continued)

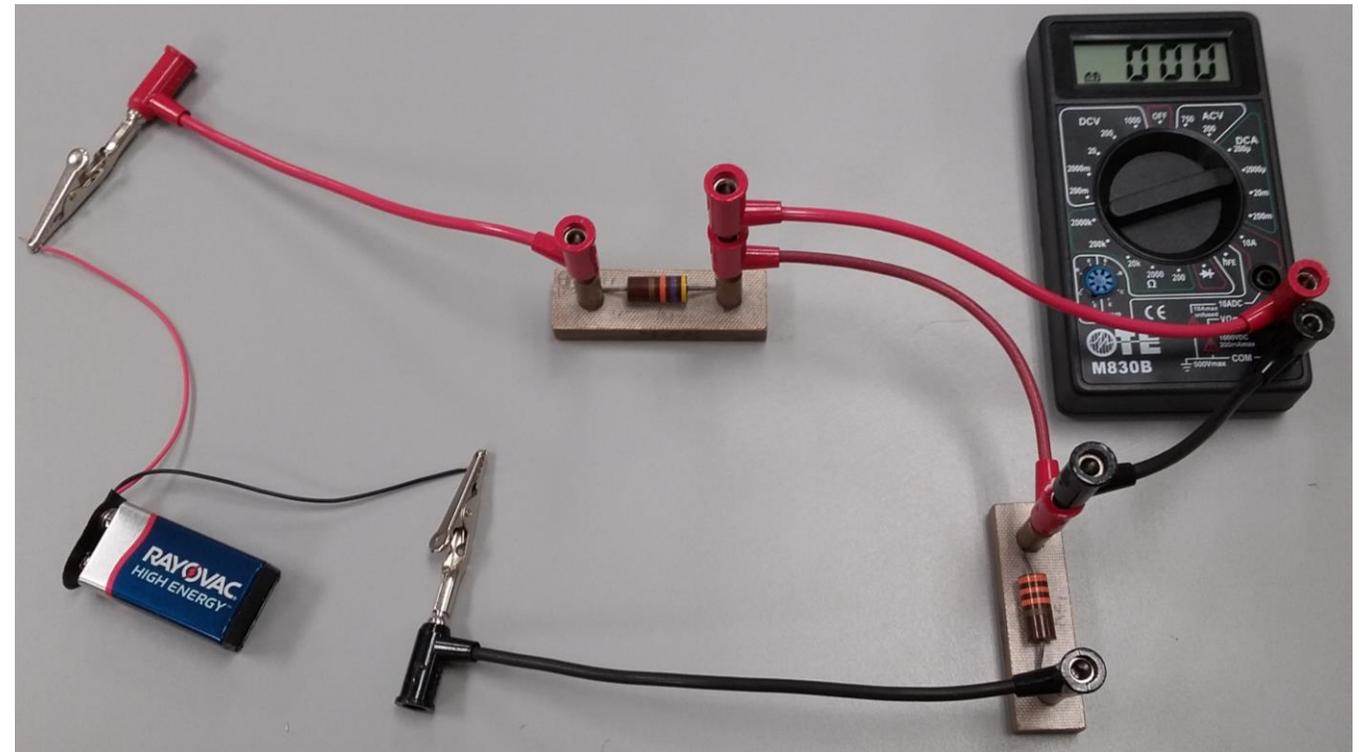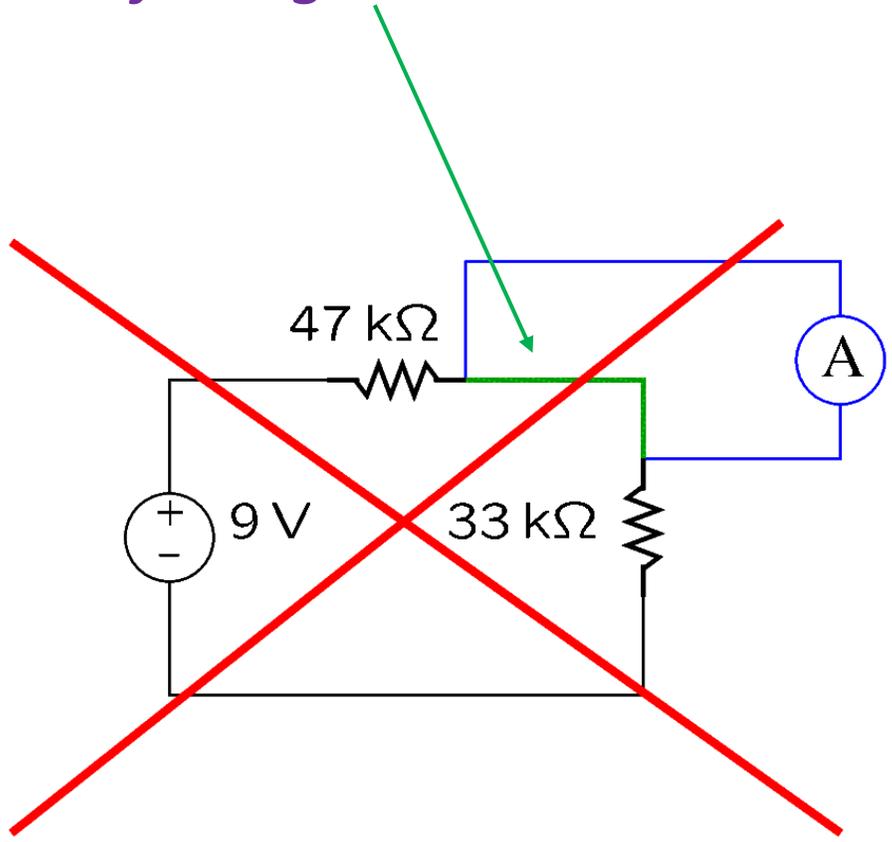- *Current cannot be measured across a wire.*
- *If the green wire is removed, the DMM will display the correct value.*



Transformers

Transformers

- A transformer is an **AC** device that transfers energy between electrically isolated circuits by means of magnetically coupled coils of wire.
- A transformer consists of several coils placed on the same magnetic core.
- Power is applied to the *primary* coil of the transformer and is transmitted by means of the magnetic field to the other coils, which are called *secondary* coils.

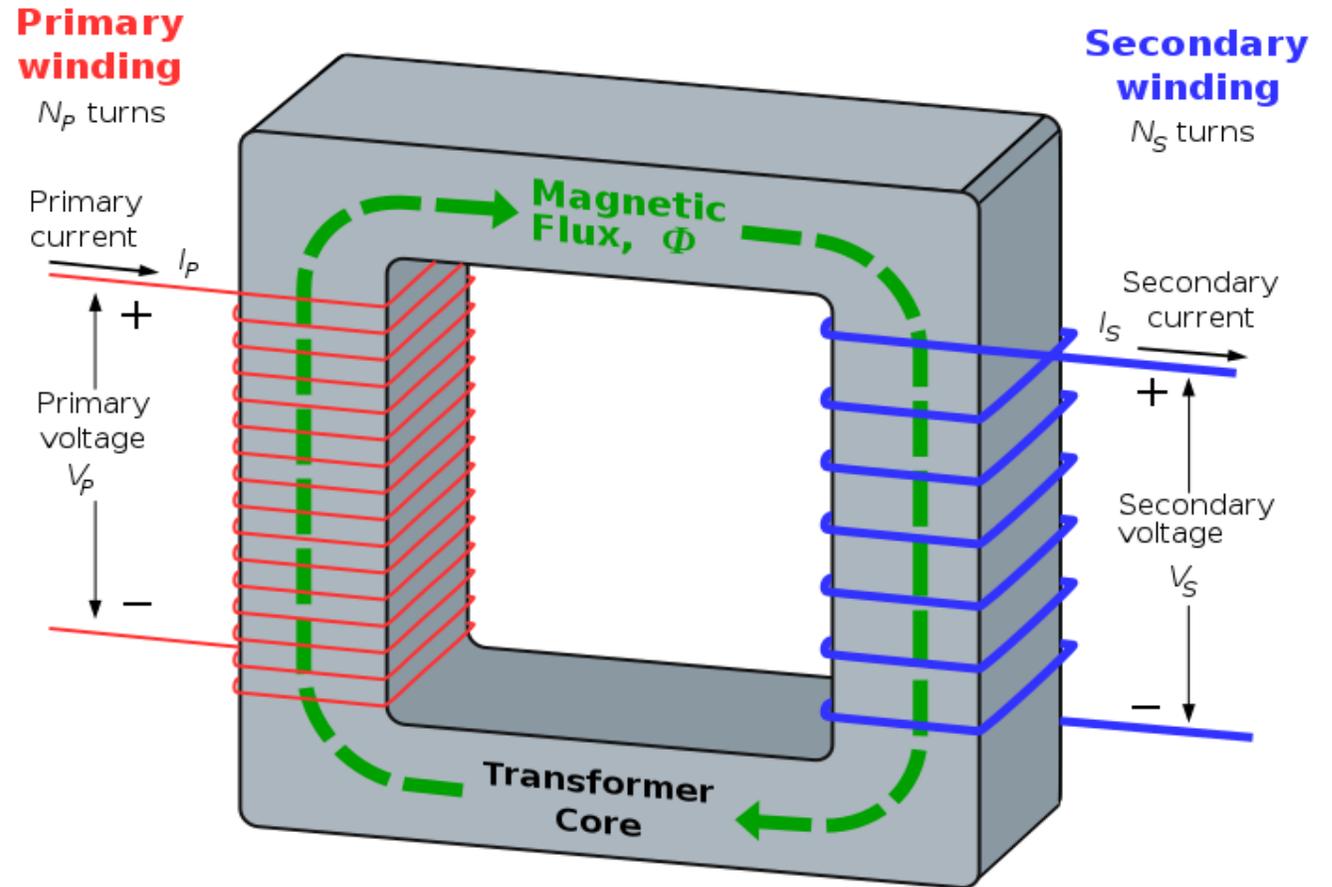


Figure downloaded from <http://en.wikipedia.org/wiki/Transformer>


Transformers

- The symbol of a transformer is shown in the figure.
- Typically, transformers transfer energy at different voltage levels; a transformer can reduce or increase the input voltage.
- Ideally,

$$\frac{V_P}{V_S} = \frac{I_S}{I_P} = \frac{N_P}{N_S}$$

where

- V_P and V_S are the rms values of the primary and secondary voltages.
 - I_P and I_S are the rms values of the primary and secondary currents.
 - N_P and N_S are the number of turns of the primary and secondary coils.
- For example, if $N_P = 800$, $N_S = 80$, and $V_p = 120\text{ V}$, then $V_S = 12\text{ V}$.
 - For example, if $N_P = 1000$, $N_S = 50$, and $I_S = 12\text{ A}$, then $I_P = 600\text{ mA}$.

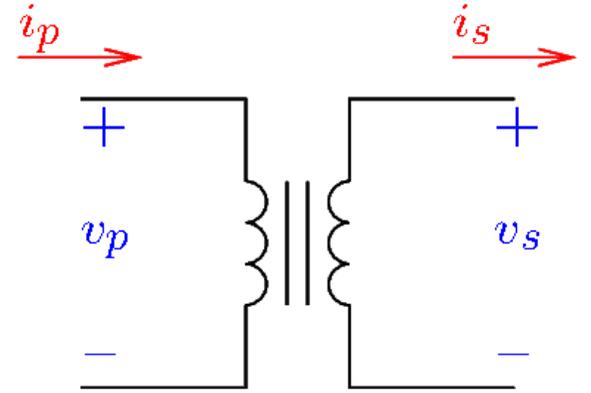

Transformers


- Transformers may have more than one secondary coil.
- Under simplifying assumptions, the operation of a transformer with m secondary coils is described by the equations:

$$\frac{V_P}{V_{S1}} = \frac{N_P}{N_{S1}} \quad \frac{V_P}{V_{S2}} = \frac{N_P}{N_{S2}} \quad \dots \quad \frac{V_P}{V_{Sm}} = \frac{N_P}{N_{Sm}}$$

$$N_P I_P = N_{S1} I_{S1} + N_{S2} I_{S2} + \dots + N_{Sm} I_{Sm}$$

where

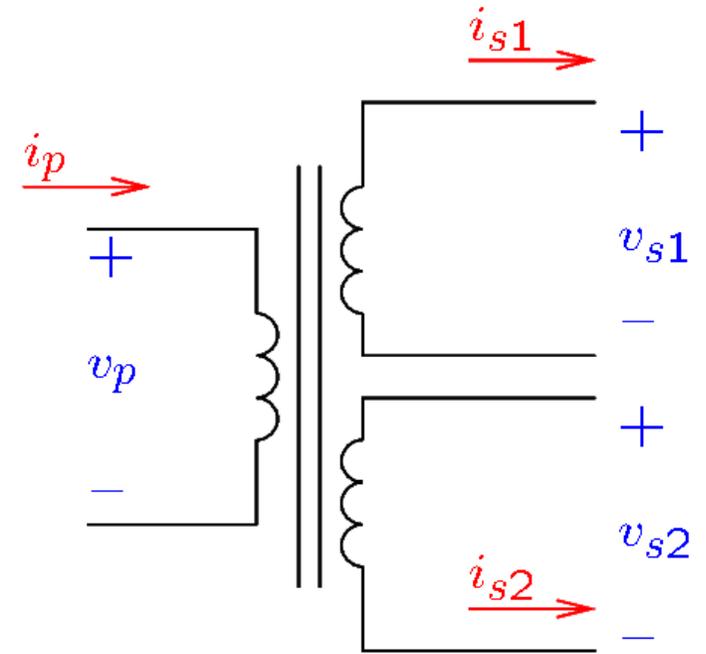- $V_P, V_{S1}, \dots, V_{Sm}$ are the rms values of the primary and secondary voltages.
- $I_P, I_{S1}, \dots, I_{Sm}$ are the rms values of the primary and secondary currents.
- $N_P, N_{S1}, \dots, N_{Sm}$ are the number of turns of the primary and secondary coils.



Clamp-on Ammeters

- Clamp-on ammeters measure the current of a conductor without physical contact.
- Some clamp-on ammeters use Hall sensors to measure the magnetic field generated by the current of the conductor. They can work with both DC and AC.
- Other clamp-on ammeter operate on the principle of the transformer: the measured conductor forms the primary, while an internal coil forms the secondary. Such ammeters work only with AC.
- Although very convenient for making rapid current measurements, clamp-on ammeters are limited to relatively high current levels.



Clamp-on Ammeters

- Current is measured correctly when the conductor goes between the two jaws of the instrument.



Jaws

